

Recap


- Ohm's law and resistance $V=IR$
- Voltage sources
- Current sources
- Kirchoff's laws $\sum_{\text{node}} \mathbf{I}_n = 0$ KCL
- $\sum_{\text{loop}} \mathbf{V}_n = 0$ KVL
- Passive sign convention

Example

$$R_1 = 3\text{k}\Omega$$

$$R_2 = 2\text{k}\Omega$$

$$R_3 = 6\text{k}\Omega$$

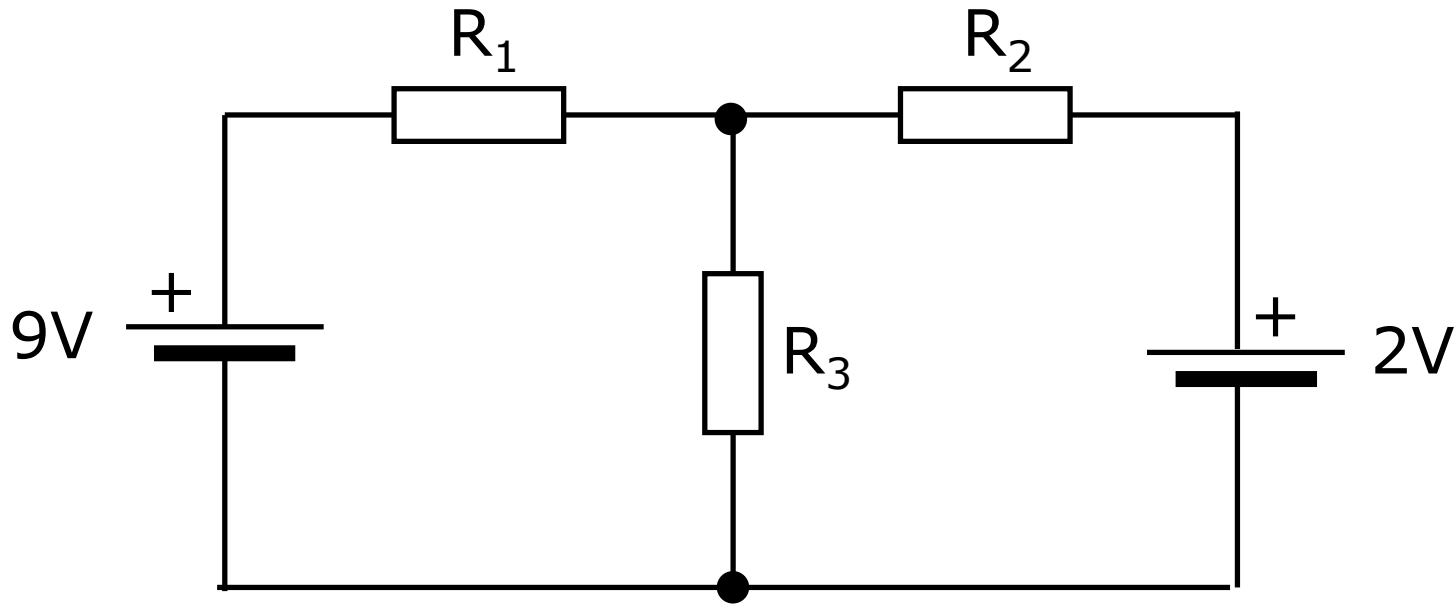

This lecture

Methods/tricks for solving circuits

- Mesh currents
- Node voltages
- Superposition
- Thevenin's theorem
- Norton's theorem

Measurements and power extraction

- Measuring voltage
- Measuring current
- Power extraction and impedance matching

Mesh currents

1. Label loop currents in all interior loops
2. Apply KVL around each loop
Using **passive sign convention** and using KCL to get currents in shared sections
3. Solve for loop currents and use these to obtain everything else.

Node voltages

1. Choose a ground node and label all other nodes.

2. Apply KCL to each node.

The currents can usually be directly written down as a $\Delta V/R$.


3. Solve for node voltages and use these to obtain everything else.

Superposition

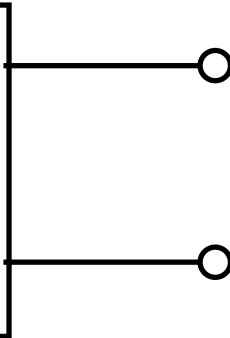
1. A linear circuit with more than one current/voltage source can be analysed by considering one source at a time.
2. When analysing just one source replace other
 - Current sources with a break
 - Voltages sources with a wire
3. The total response of the circuit will be the sum of the individual responses.
 - Make sure you label everything with the same directions

Thevenin's theorem

Any **linear** network of voltage/current sources and resistors



≡

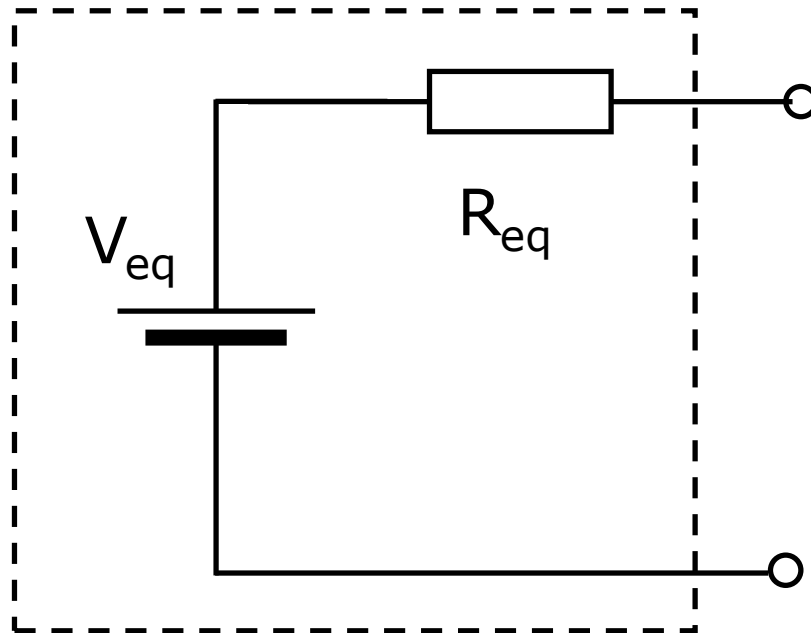

Equivalent circuit


$$V_{eq} = V_{\text{open-circuit}}$$

$$R_{eq} = \frac{V_{eq}}{I_{\text{short-circuit}}}$$


Norton's theorem

Any linear network of voltage/current sources and resistors

Thevenin

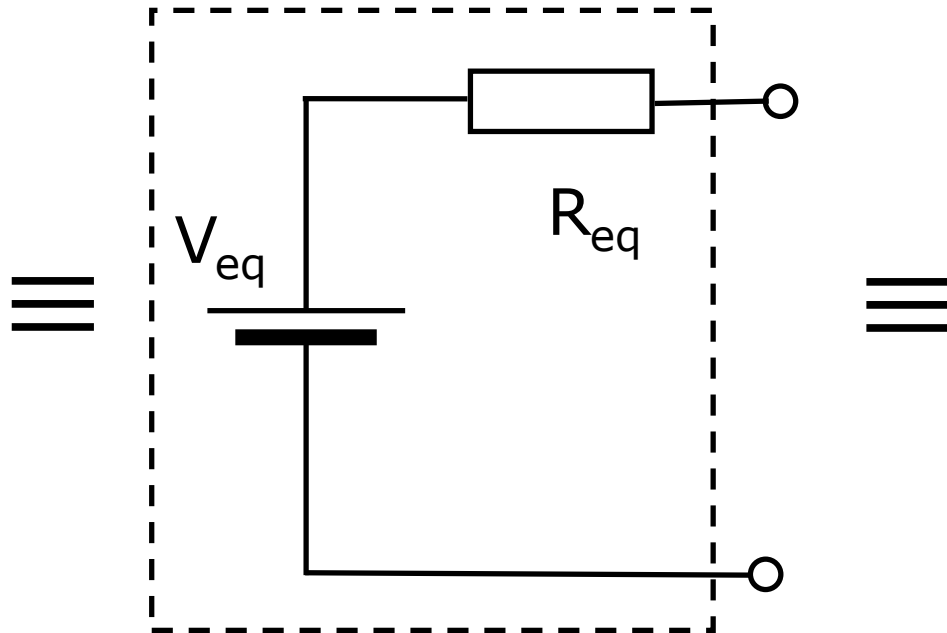

Norton

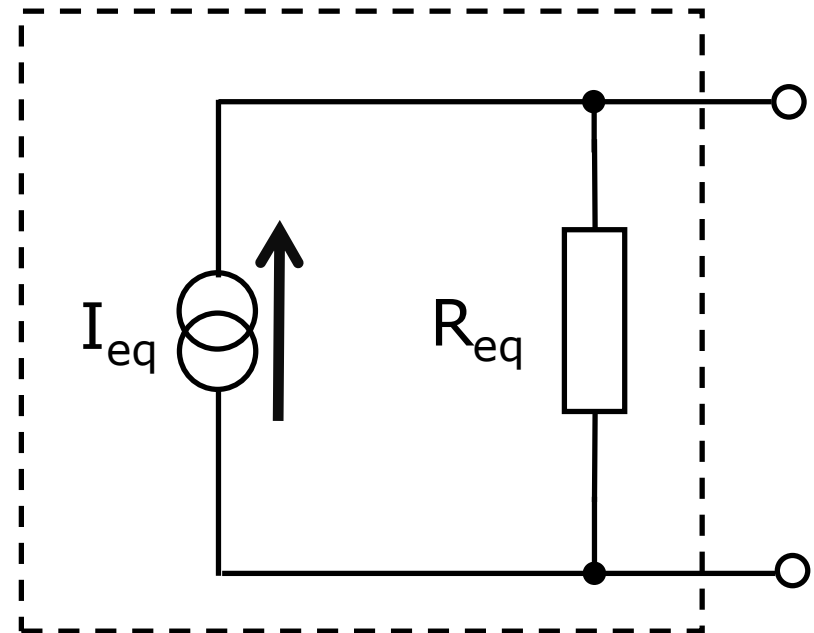


$$I_{eq} = \frac{V_{eq}}{R_{eq}}$$

Methods/tricks for solving circuits

- Mesh currents
- Node voltages
- Superposition
- Thevenin's theorem
- Norton's theorem

Which trick to use?

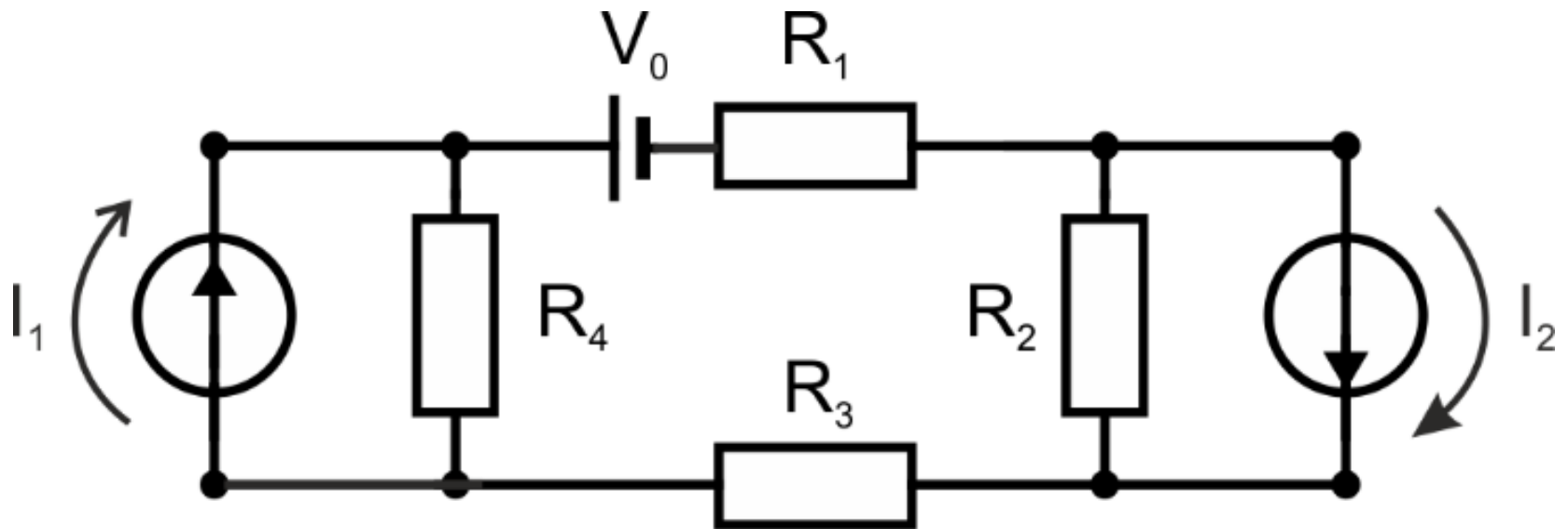


Measuring circuit voltages and currents

Voltage measurements: need $R_{in} \gg R_{eq}$

$10M\Omega$




$1M\Omega$

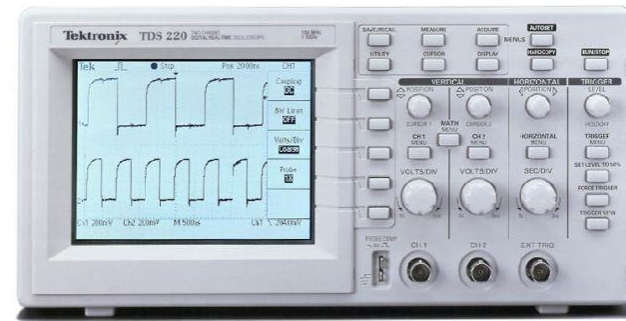

Current measurement: need $R_{in} \ll R_{eq}$

Matching: maximum power transfer

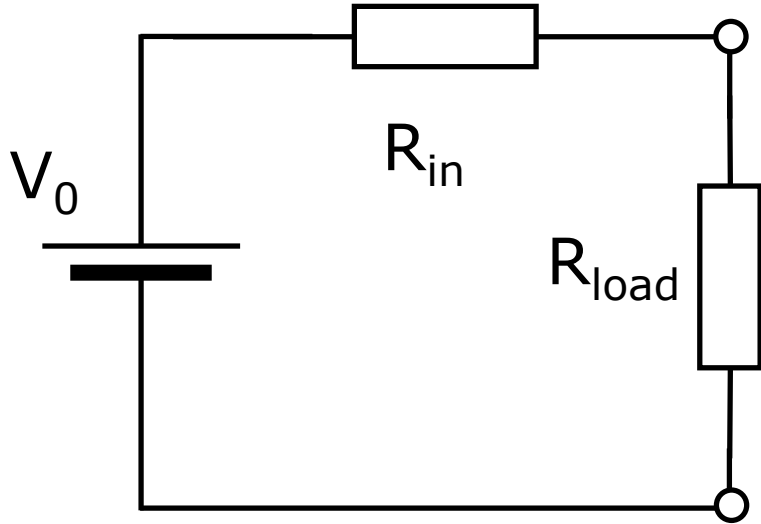

Find R_L to give maximum power in load

$$P = \frac{V_L^2}{R_L} = V_0^2 \frac{R_L^2}{(R_{in} + R_L)^2} \frac{1}{R_L}$$

$$\text{Max when } \frac{dP}{dR_L} = 0 \Rightarrow R_L = R_{in}$$

Maximum power transfer when $R_L = R_{in}$

Note – power dissipated half in R_L and half in R_{in}

Circuits have Consequences

- Problem:
 - My old speakers are 60W speakers.
 - Special 2-4-1 deal at El-Cheap-0 Acoustics on 120W speakers!!
 - (“Offer not seen on TV!”)
 - Do I buy them?
- Depends! 4W, 8W, or 16W speakers?
- **Why does this matter?**

