

Recap

- Resistors ($V=IR$), voltage and current sources
- Kirchoff's laws $\text{KCL } \sum_{\text{node}} \mathbf{I}_n = 0$ $\text{KVL } \sum_{\text{loop}} \mathbf{V}_n = 0$
- Techniques
 - Mesh currents
 - Node voltages
 - Superposition
 - Thevenin theorem
 - Norton theorem
- Impedance matching

Today

- Capacitors and inductors
- Transient circuits

Capacitors




Capacitors store charge

Definition: $C = \frac{Q}{V}$

Units: farad [F]=[CV⁻¹]=[AsV⁻¹]

more usually μF , nF, pF

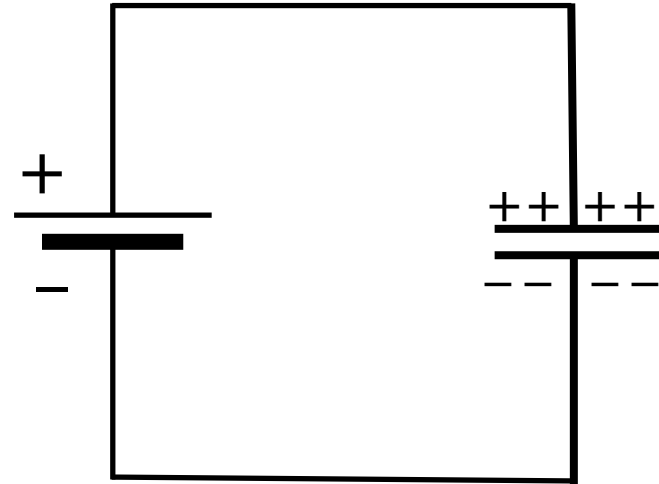

$$Q = CV$$

$$I = \frac{dQ}{dt} \longrightarrow I = C \frac{dV}{dt}$$

Parallel plate capacitor

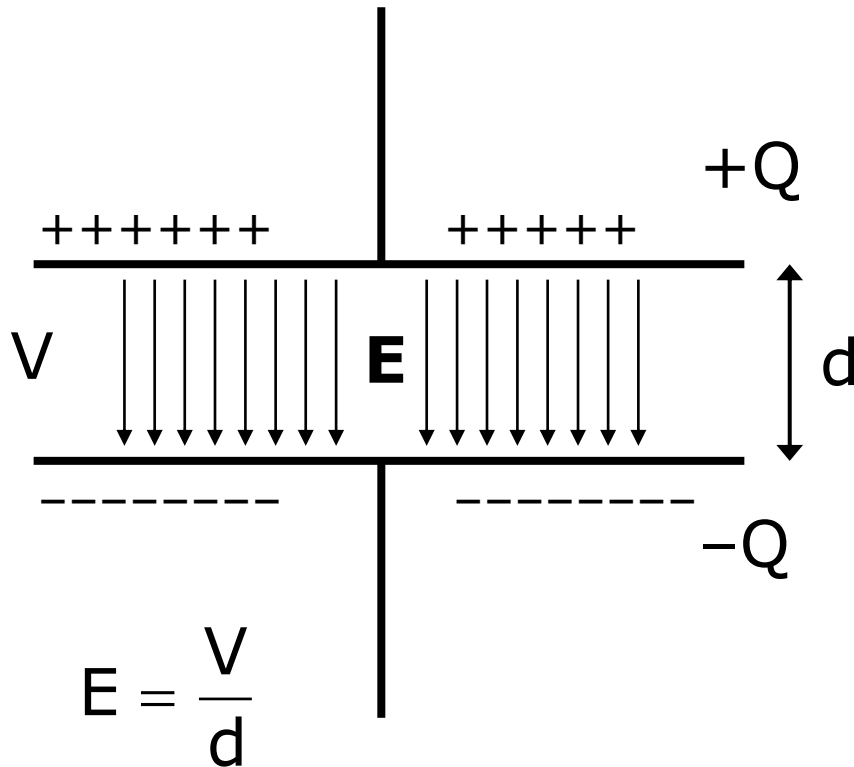
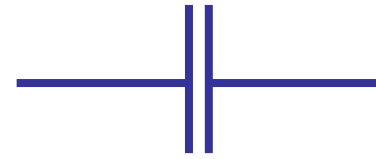





plate area

$$C = \frac{\epsilon A}{d}$$

Dielectric permittivity
 $\epsilon = \epsilon_r \epsilon_0$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ CV}^{-1} \text{ m}^{-1}$$

Capacitor types

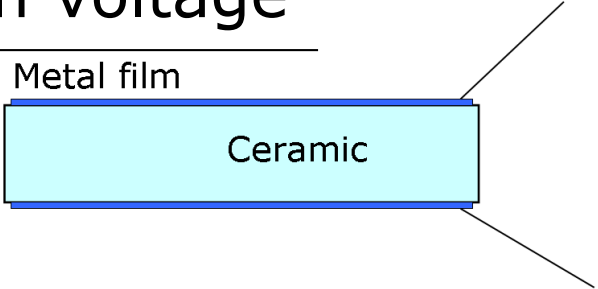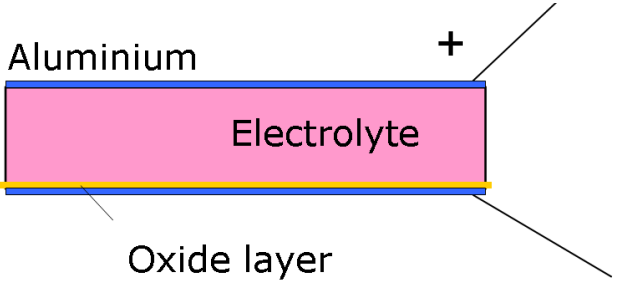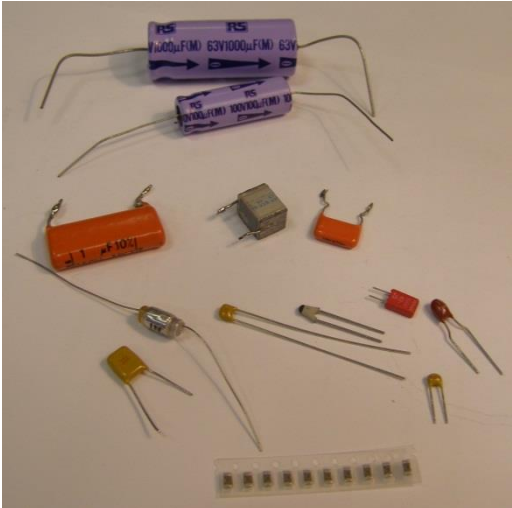
	Range	Maximum voltage	
Ceramic	1pF–1μF	30kV	
Mica	1pF–10nF	500V	(very stable)
Plastic	100pF–10μF	1kV	
Electrolytic	0.1μF–0.1F	500V	
Parasitic	~pF		

Polarised


Capacitors

Capacitors in parallel:
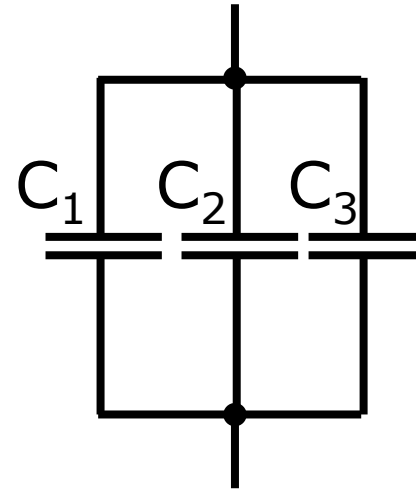
$$C_{\text{Total}} = \sum_n C_n = C_1 + C_2 + C_3 \dots$$



Capacitors in series:

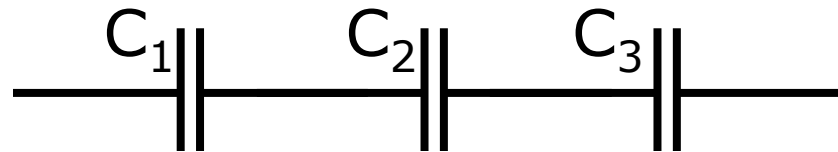

$$\frac{1}{C_T} = \sum_n \frac{1}{C_n} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots$$


Capacitors – energy stored

$$\begin{aligned} W &= \int_0^t P(t') dt' = \int_0^t I(t') V(t') dt' = \int_0^t C \frac{dV(t')}{dt'} V(t') dt' \\ &= C \int_0^V V' dV' = \frac{1}{2} CV^2 \end{aligned}$$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{Q^2}{2C}$$

Energy stored as electric field

RC circuits

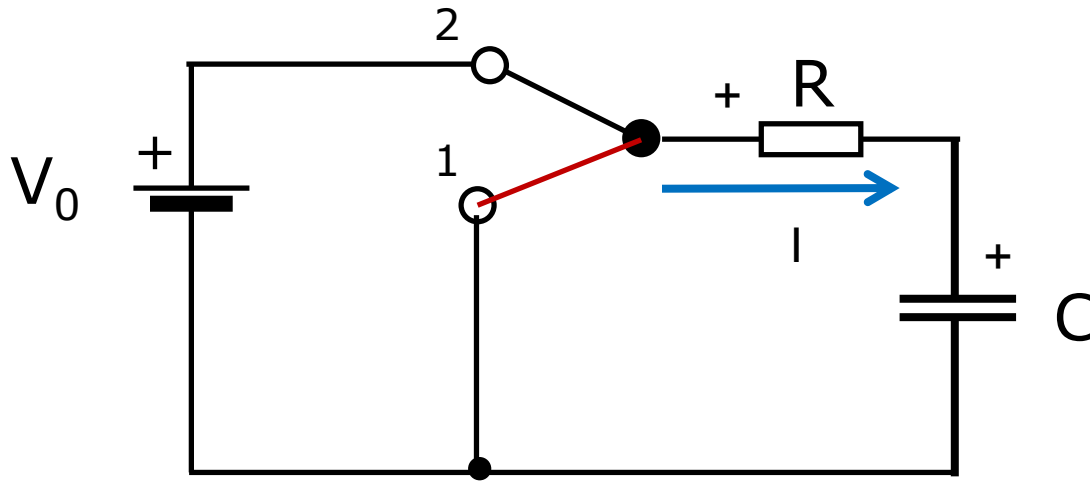


- Switch in Position "1" for a long time.
- Then instantly flips at time $t = 0$.
- How do we analyse this?

and Apply KVL

ALWAYS start by asking these three questions:

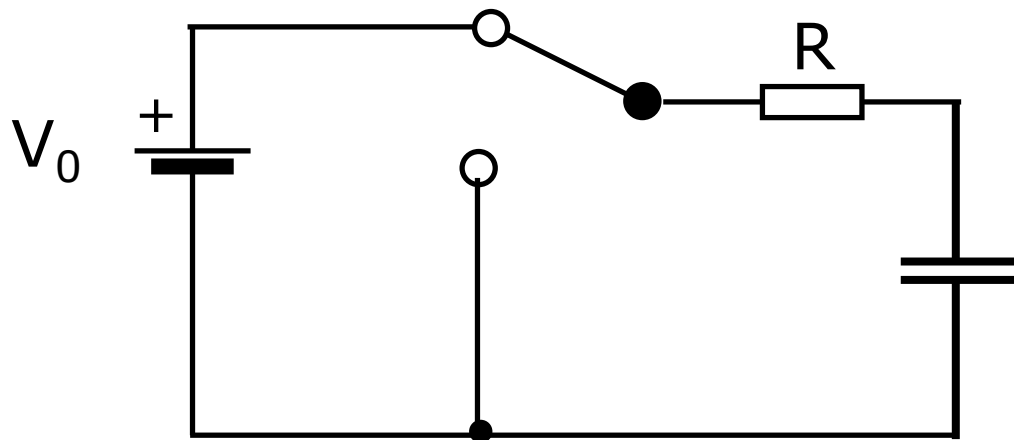
1. What does the Circuit do up until the switch flips? (Switch has been at pos. 1 for a VERY long time. **easy**)
2. What does the circuit do a VERY long time AFTER the switch flips? (**easy**)
3. What can we say about the INSTANT after switch flips? (**easy if you know the rule**)

It is impossible to change the voltage on a capacitor instantly!



$$I(t) = \frac{V_0}{R} e^{-t/\tau}$$


$$\tau = RC$$

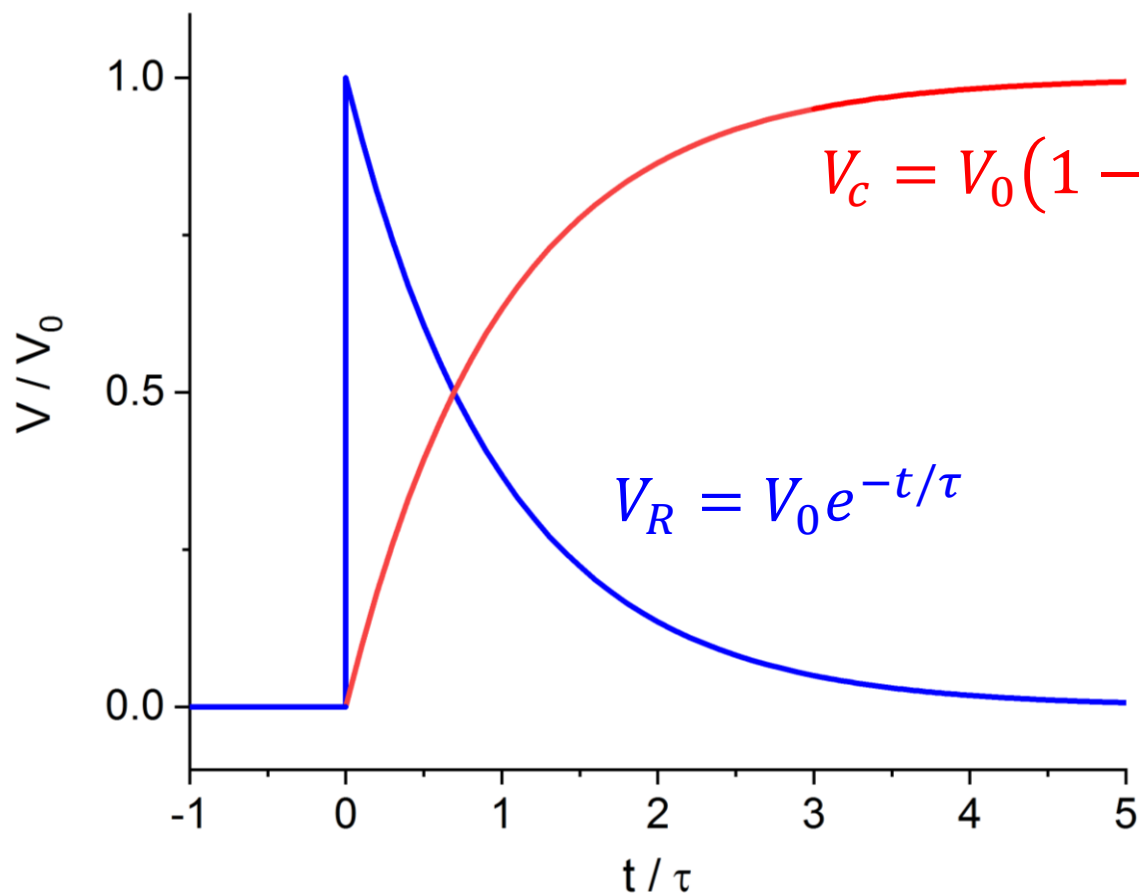

Inductors



Oppose a change in current

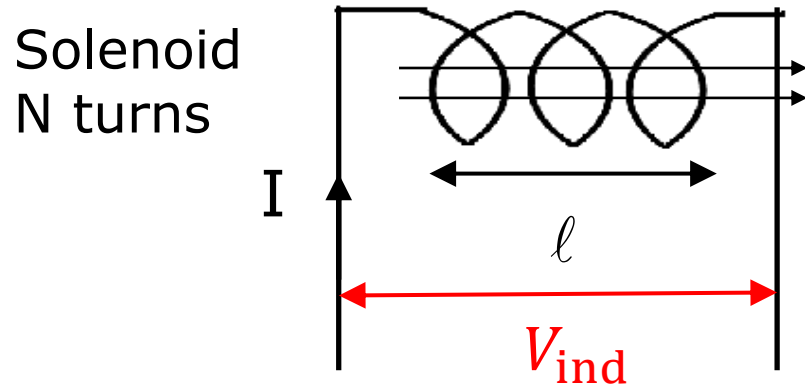

$$B = \frac{\mu_0 NI}{l}$$

$$\Phi = \int B \cdot dA = BAN = \frac{\mu_0 N^2 A}{l} I$$

Try to change I:

Electromagnetic induction

- Faraday's law;
- Lenz's law - V_{ind} will oppose change

$$V_{\text{ind}} = \frac{d\Phi}{dt} = L \frac{dI}{dt}$$


inductance

$$L = \frac{\mu_0 N^2 A}{l}$$


Units: henrys [H] = [VsA⁻¹]

Mutual inductance

Self Inductance

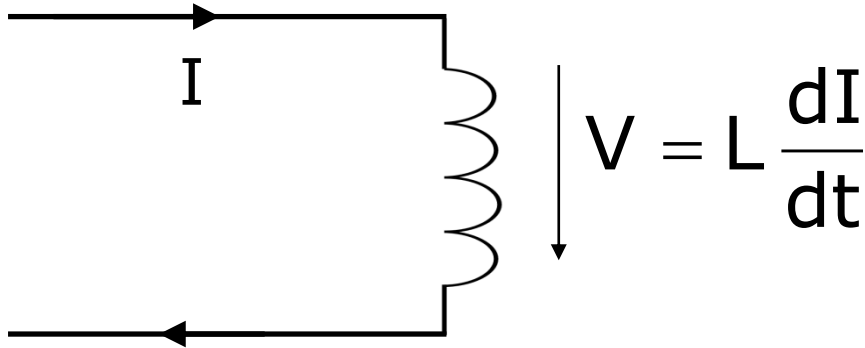





Mutual Inductance

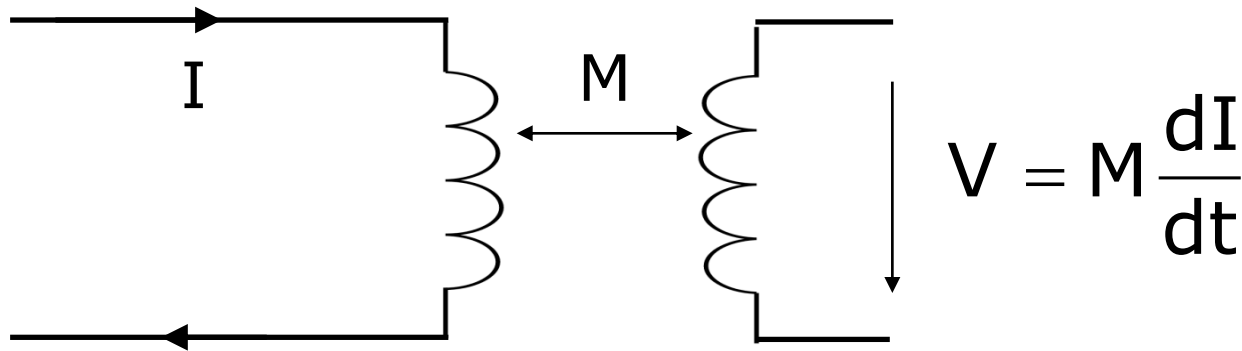

Inductors

Wire wound coils - air core

- ferrite core

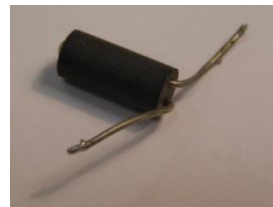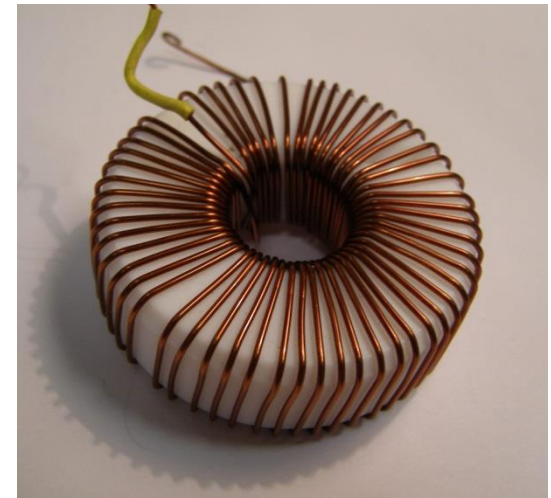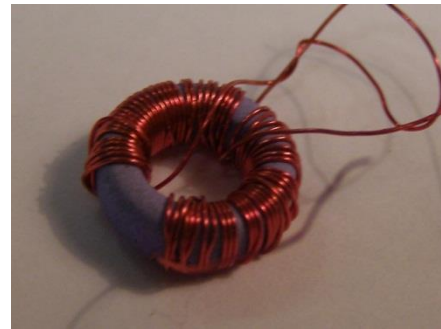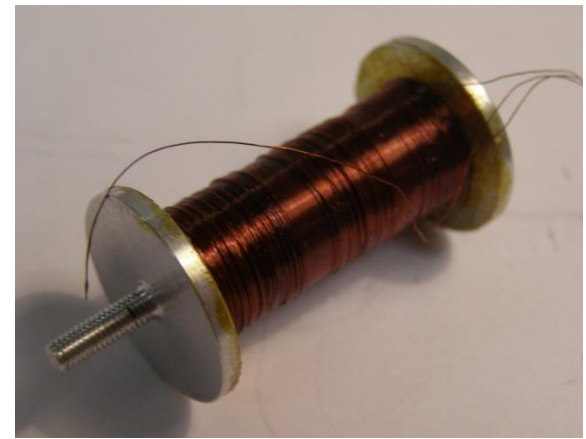


Wire loops

Straight wire



Inductors

Inductors in series:

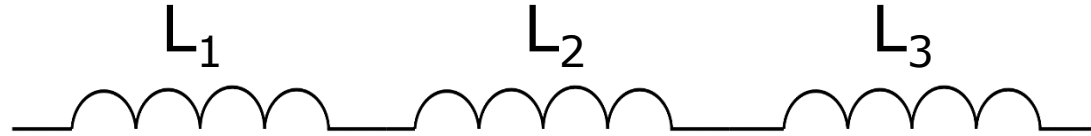


$$L_{\text{Total}} = L_1 + L_2 + L_3 \dots$$

$$L_T = \sum_n L_n$$

Inductors in parallel
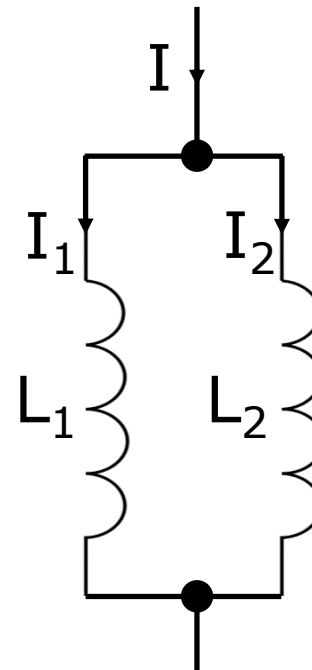
$$\begin{aligned} \frac{1}{L_T} &= \sum_n \frac{1}{L_n} \\ &= \frac{1}{L_1} + \frac{1}{L_2} + \dots \end{aligned}$$




Inductors – energy stored

$$\begin{aligned}W &= \int_0^t P(t') dt' \\&= \int_0^t I(t') V(t') dt' \\&= \int_0^t I(t') L \frac{dI(t')}{dt} dt' \\&= L \int_0^I I dI' \\&= \frac{1}{2} LI^2\end{aligned}$$

Energy stored as magnetic field

RL circuits

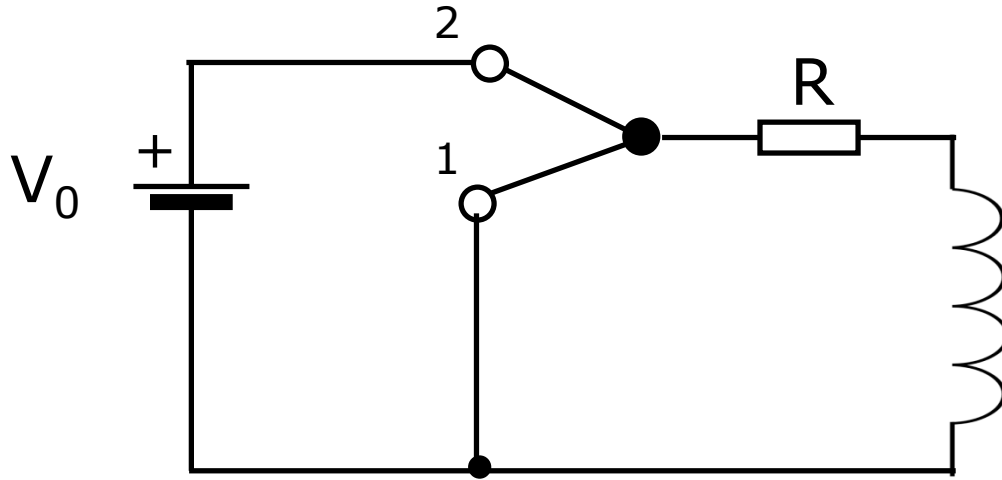


- Switch in Position "1" for a long time.
- Then instantly flips at time $t = 0$.
- How do we analyse this?

and Apply KVL

ALWAYS start by asking these three questions:

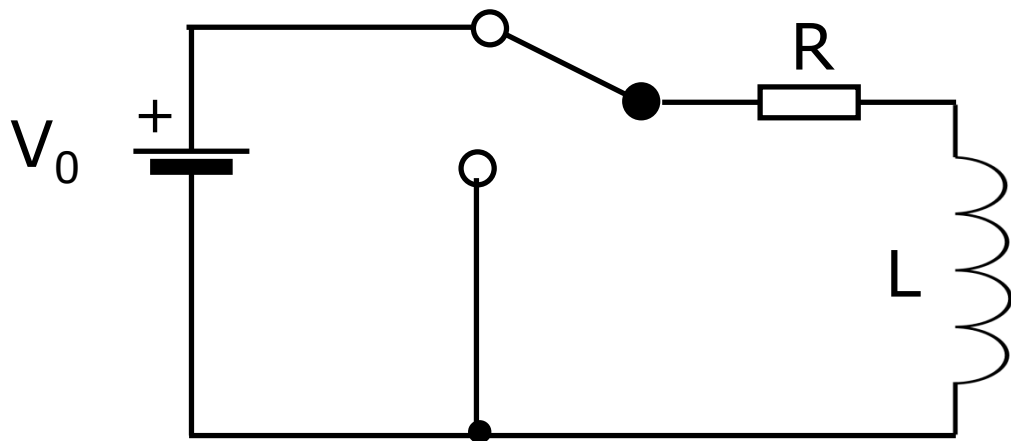
1. What does the Circuit do up until the switch flips?
(Switch has been at pos. 1 for a VERY long time. *easy*)
2. What does the circuit do a VERY long time AFTER the switch flips? (*easy*)
3. What can we say about the INSTANT after switch flips? (*easy if you know the rule*)


It is impossible to change the current on a inductor instantly!



$$I(t) = \frac{V_0}{R} \left(1 - \exp\left(-\frac{t}{\tau}\right) \right)$$

$$\tau = \frac{L}{R}$$

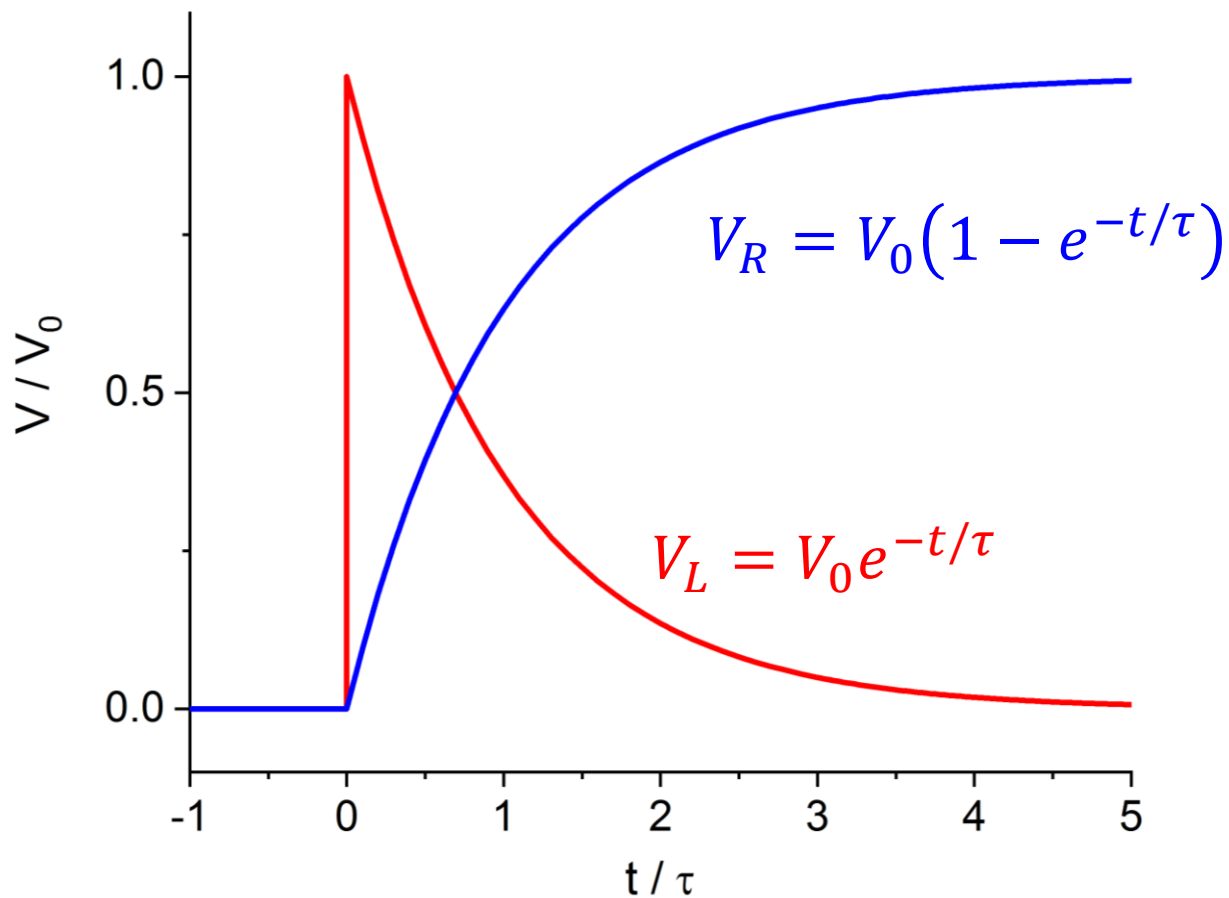

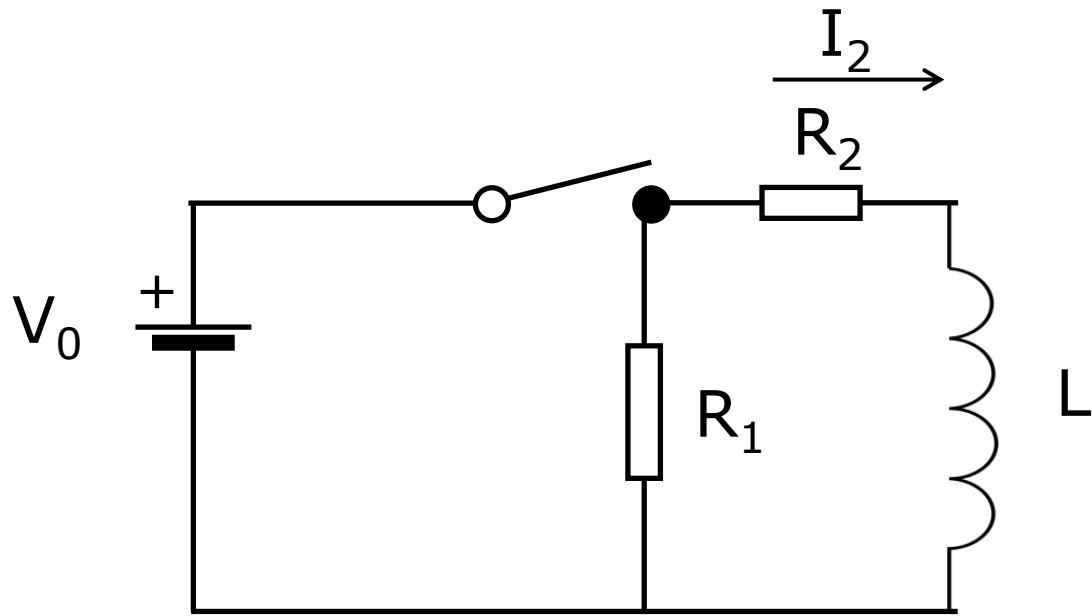

$t < 0$ switch closed $I_2 = ?$

$t = 0$ switch opened

$t > 0$ $I_2(t) = ?$

voltage across $R_1 = ?$

Let R_1 get very large:

What happens to V_L ?

Do through if time otherwise try at home