

# 1st-year Circuits

## Lectures 3 and 4

Robert Smith

Michaelmas 2019

### 6 Capacitors

- Capacitors store charge. The capacitance  $C$  is defined as the charge stored per unit voltage  $C = \frac{Q}{V}$ ; it is measured in Farads (F) or more usually in  $\mu\text{F}$ , nF or pF.
- Capacitors in series add as  $\frac{1}{C_T} = \sum_n \frac{1}{C_n}$  and in parallel as  $C_T = \sum_n C_n$ .
- The energy stored on a capacitor is given by  $W = \frac{1}{2}CV^2$ . The energy is stored in the electric field.

### 7 Inductors

- Inductors oppose a change in current. They are usually coils of wire; a current passing through them results in a linked magnetic field flux  $\Phi$ ; changing the current through the circuit means changing the magnetic flux which (via Faraday's law) results in an induced voltage:  $V = \frac{d\Phi}{dt}$  which opposes the change in current. The inductance is defined via  $V = L\frac{dI}{dt}$ , it tells you the voltage that will be induced if the current is changed at 1 Ampere per second. Inductance is measured in Henrys (H).
- Inductors in series add as  $L_T = \sum_n L_n$  and in parallel as  $\frac{1}{L_T} = \sum_n \frac{1}{L_n}$ .
- The energy stored on a inductor is given by  $W = \frac{1}{2}LI^2$ . The energy is stored in the magnetic field.


### 8 Transients in RC and RL circuits

A sudden change in a RC (resistor/capacitor) or RL (resistor / inductor) circuit, such as closing a switch, results in a time-varying transient response. Such problems can be tackled as follows:

- Define current directions and apply the passive sign convention as normal.
- Apply Kirchoff's laws, remembering that for a capacitor  $V = \frac{Q}{C}$  and for an inductor  $V = L\frac{dI}{dt}$ .
- This will lead to a (or a set of) differential equation(s). Solve these equations subject to the appropriate boundary conditions (ask what is the situation at  $t = 0$  and at  $t = \infty$ ) taking into account that:
  - it is impossible to change the voltage on a capacitor instantly (because charge has to build up and so that would require infinite current),
  - it is impossible to change the current on a inductor instantly (because that would result in infinite voltage).
- For a series RC and RL circuit the transient response is characterised by a decay/growth of current/voltage with a time constants of  $\frac{1}{RC}$  and  $\frac{L}{R}$  respectively.
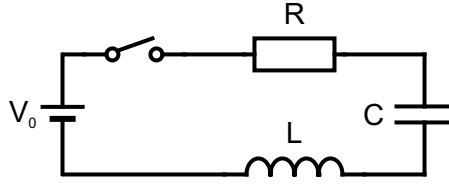
## 9 LCR series circuit

Consider the circuit below. The capacitor is initially uncharged and at time  $t = 0$  the switch is closed.



Applying KVL we find:

$$V_0 = IR + \frac{Q}{C} + L \frac{dI}{dt} \quad (1)$$

where  $Q$  is the charge on the capacitor and  $I = \frac{dQ}{dt}$  the current in the circuit. This can be re-written as

$$V_0 = L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C}Q, \quad (2)$$

or

$$0 = L \frac{d^2I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C}I. \quad (3)$$

These are equations for damped simple harmonic motion; note there is a direct equivalence with a mechanical oscillator, with the displacement  $x \mapsto Q$ , the velocity  $v \mapsto I$ , the mass  $m \mapsto L$  and the spring constant  $k \mapsto 1/C$ ,  $R$  defines the damping. The general solution of Eq. (3) is  $I = Ae^{\lambda_1 t} + Be^{\lambda_2 t}$  where  $\lambda_{1,2} = -\gamma \pm \sqrt{\gamma^2 + \omega_0^2}$  with  $\gamma = \frac{R}{2L}$  and  $\omega_0^2 = \frac{1}{LC}$ . The nature of the solution depends on  $\gamma/\omega_0$  leading to three different types of solution. In this instance, using the  $t = 0$  boundary conditions:  $I = 0$  (because of the inductor) and  $L \frac{dI}{dt} = V_0$  (because initially  $Q = 0$ ), we have the following solutions:

- Over-damped ( $\gamma > \omega_0$ )

$$I = \frac{V_0}{2L\sqrt{\gamma^2 - \omega_0^2}} \left( e^{-(\gamma - \sqrt{\gamma^2 - \omega_0^2})t} - e^{-(\gamma + \sqrt{\gamma^2 - \omega_0^2})t} \right). \quad (4)$$

- Critically damped ( $\gamma = \omega_0$ )

$$I = \frac{V_0}{L} t e^{-\gamma t}. \quad (5)$$

- Under-damped ( $\gamma < \omega_0$ )

$$I = \frac{V_0}{L\sqrt{\omega_0^2 - \gamma^2}} e^{-\gamma t} \sin \left( \sqrt{\omega_0^2 - \gamma^2} t \right). \quad (6)$$

Example solutions are shown below, where we have chosen  $C = 1 \mu\text{F}$ ,  $L = 10 \text{ mH}$  and  $R = 33, 200$  and  $600 \Omega$  leading to a fixed  $\omega_0 = 10^4 \text{ rad s}^{-1}$  and  $\gamma/\omega_0 = 1/6, 1$  and  $3$  for the under-, critical- and over-damped cases respectively.

