

Recap

- Capacitors store charge; they resist a change of voltage

$$V = \frac{Q}{C} \quad W = \frac{1}{2} CV^2$$

- Inductors oppose a change in current

$$V = L \frac{dI}{dt} \quad W = \frac{1}{2} LI^2$$


- Transient circuits

$$\tau = RC$$

Capacitor and resistor in series

$$\tau = \frac{L}{R}$$

Inductor and resistor in series

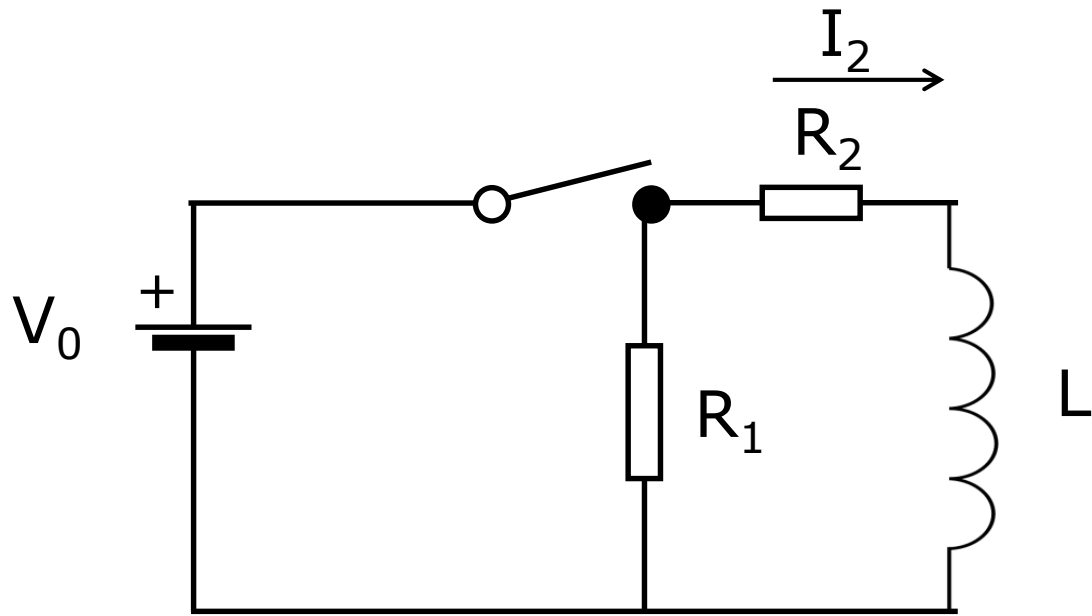

$t < 0$ switch closed $I_2 = ?$

$t = 0$ switch opened

$t > 0$ $I_2(t) = ?$


voltage across $R_1 = ?$

Let R_1 get very large:

What happens to V_L ?

LC circuit

At $t = 0$
 $Q = Q_0 = CV_0$

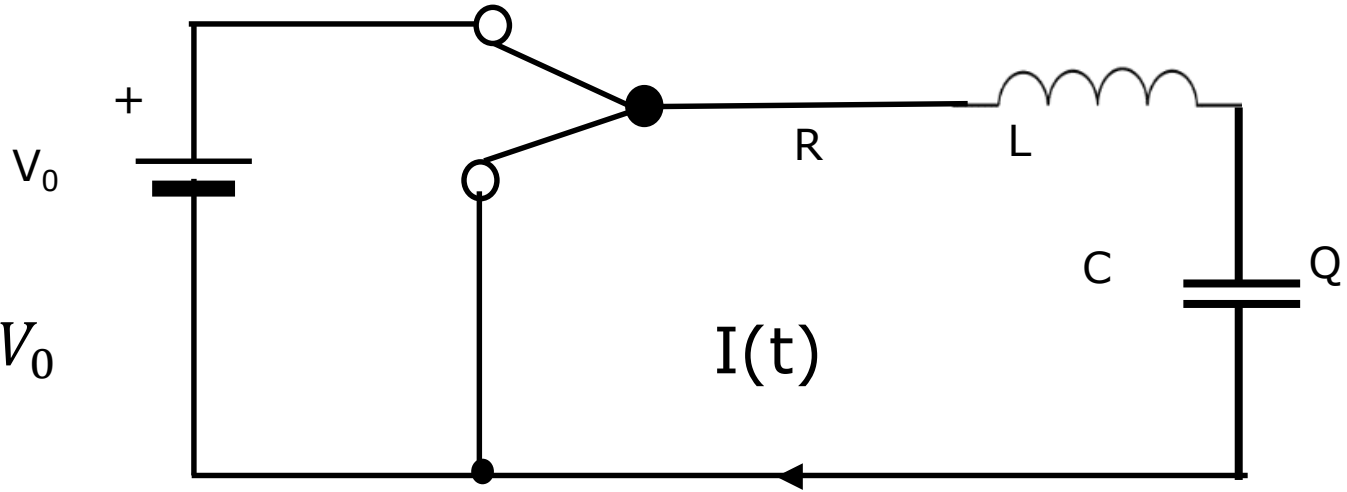


$$L \frac{dI}{dt} + \frac{Q}{C} = 0 \quad \rightarrow \quad L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0 \quad \rightarrow \quad \frac{d^2 Q}{dt^2} + \omega_0^2 Q = 0$$


$$\rightarrow Q = Q_0 \cos \omega_0 t$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

Harmonic oscillator

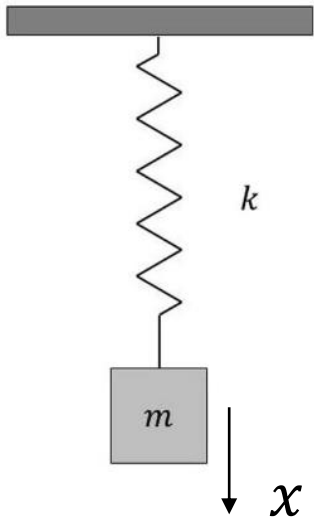

equivalent

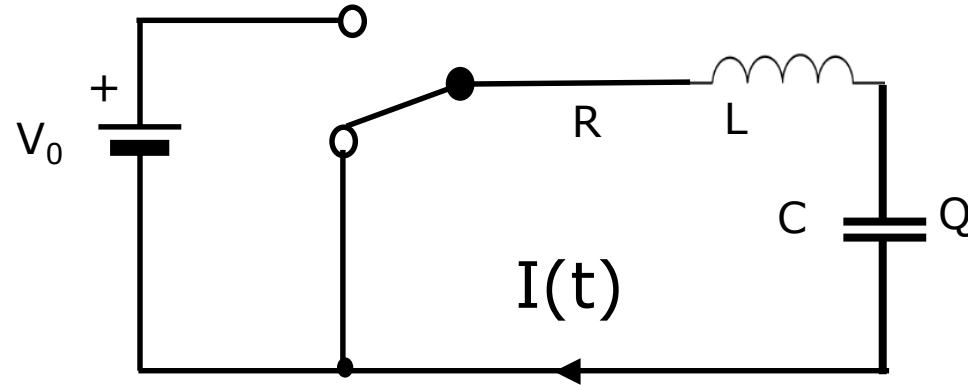


$$x \rightarrow Q$$

$$\dot{x} \rightarrow I$$

$$m \rightarrow L$$

$$k \rightarrow \frac{1}{C}$$

LCR circuit

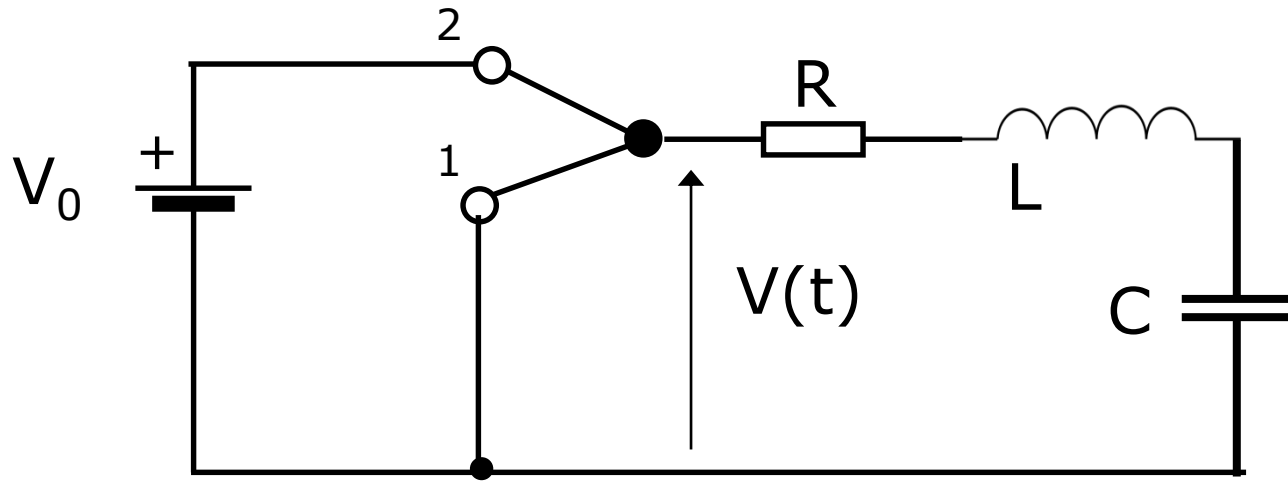

$$V(t) = \begin{cases} 0 & \text{for } t < 0 \\ V_0 & \text{for } t \geq 0 \end{cases}$$

$$I(t) = 0 \text{ for } t < 0$$

KVL

$$t \geq 0$$

$$V_R + V_L + V_C = V_0$$


Component Laws

$$IR + L \frac{dI}{dt} + \frac{Q}{C} = V_0$$


Get Rid of "Q"

$$\frac{d^2I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$$

Damped harmonic oscillator

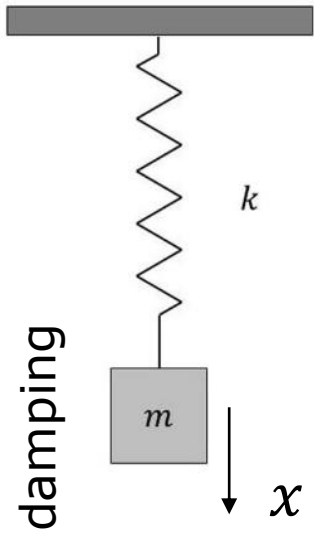

equivalent

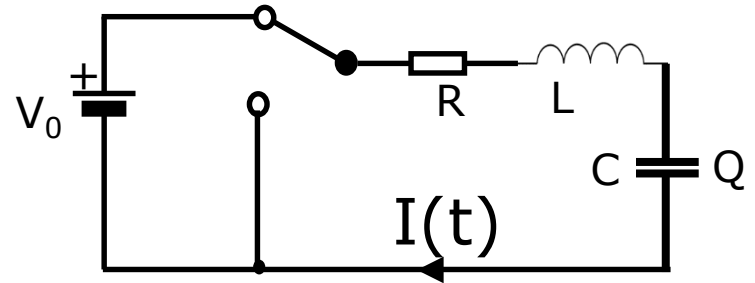

$$x \rightarrow Q$$


$$\dot{x} \rightarrow I$$

$$m \rightarrow L$$

$$k \rightarrow \frac{1}{C}$$

$$\text{Damping} \rightarrow R$$

LCR circuit – initial conditions

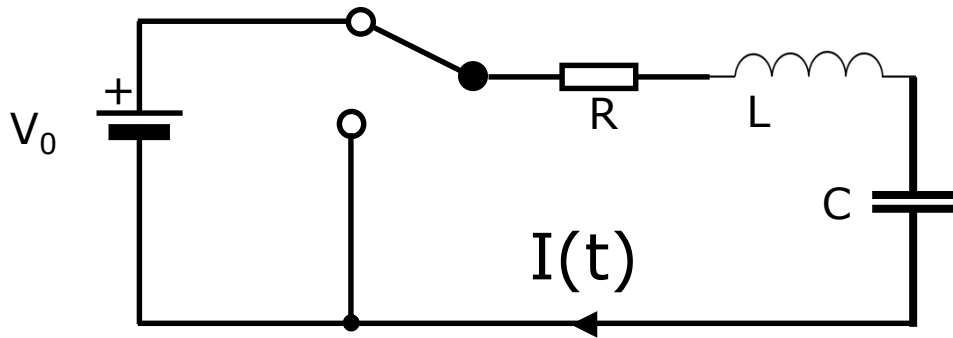

It is impossible to change the current on a inductor instantly!


$$I(t = 0) = 0$$

It is impossible to change the voltage on a capacitor instantly!

$$L \frac{dI}{dt} \Big|_{t=0} = V_0$$

Also using $I=0$

LCR circuit

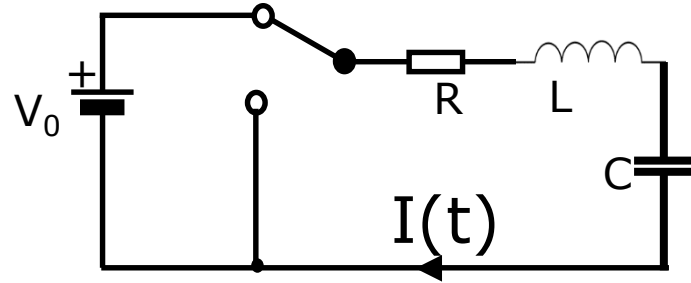

Equation for I

$$\frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = 0$$



$$\frac{d^2 I}{dt^2} + 2\gamma \frac{dI}{dt} + \omega_0^2 I = 0 \quad \gamma = \frac{R}{2L} \quad \omega_0^2 = \frac{1}{LC}$$

general solution

$$I = Ae^{\lambda_1 t} + Be^{\lambda_2 t} \quad \lambda_{1,2} = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

Form of solution depends on $\frac{\gamma}{\omega_0}$

Over-damped ($\gamma > \omega_0$)

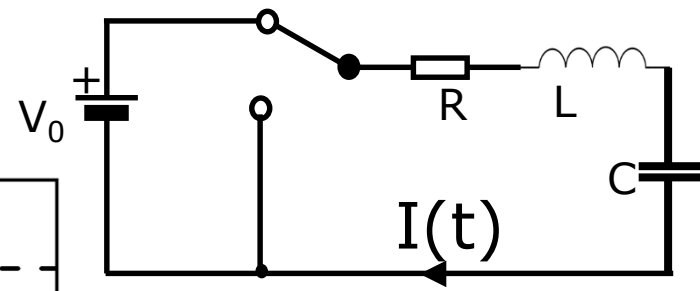
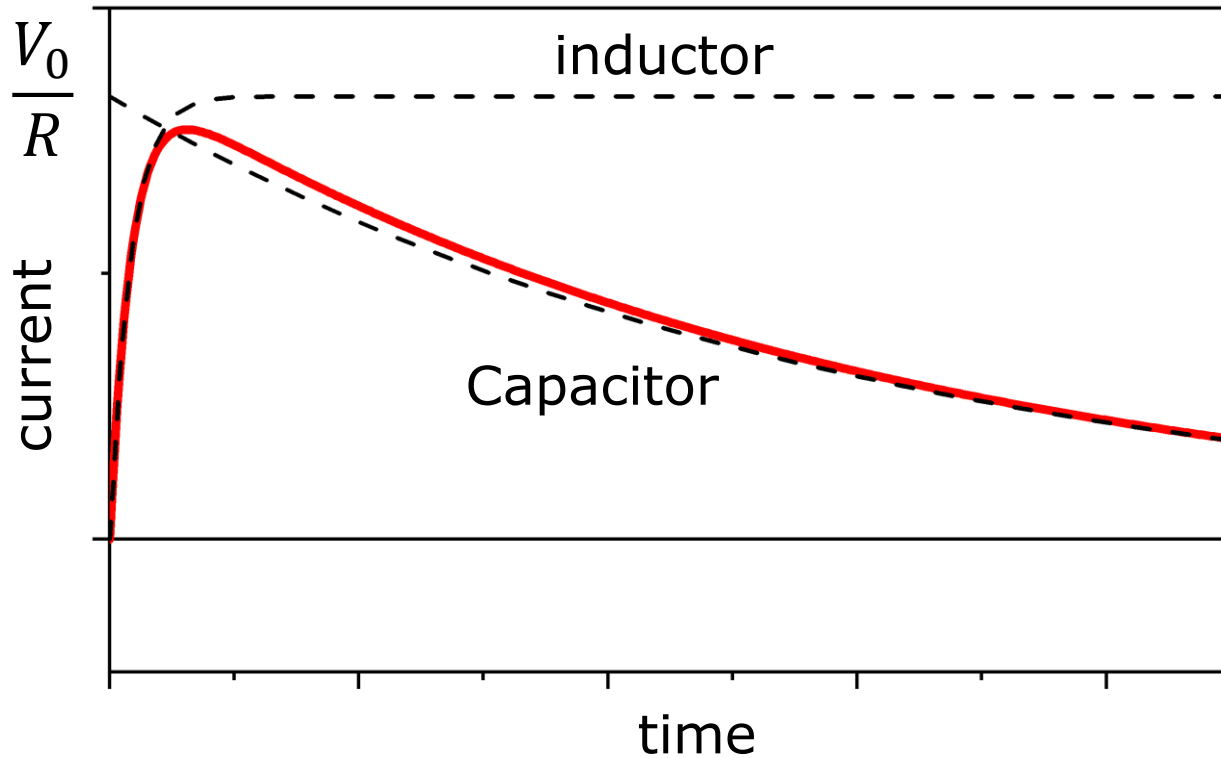


$$\lambda_{1,2} = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}$$

$$I = \frac{V_0}{R\sqrt{1 - \omega_0^2/\gamma^2}} \left[\exp\left(-\left(1 - \sqrt{1 - \frac{\omega_0^2}{\gamma^2}}\right)\gamma t\right) - \exp\left(-\left(1 + \sqrt{1 - \frac{\omega_0^2}{\gamma^2}}\right)\gamma t\right) \right]$$



$$I \approx \frac{V_0}{R} \left[\exp\left(-\frac{t}{\tau_C}\right) - \exp\left(-\frac{t}{\tau_L}\right) \right] \quad (\gamma \gg \omega_0) \quad \tau_C = RC \quad \tau_L = \frac{L}{R}$$

Critically-damped ($\gamma = \omega_0$)

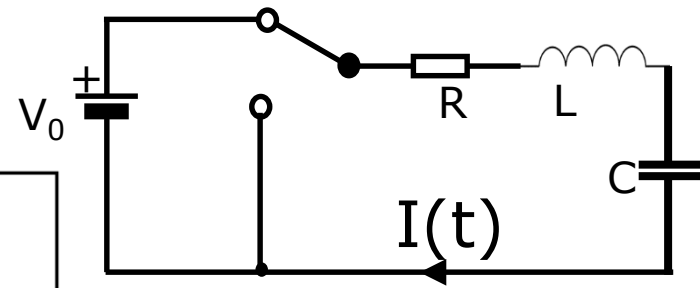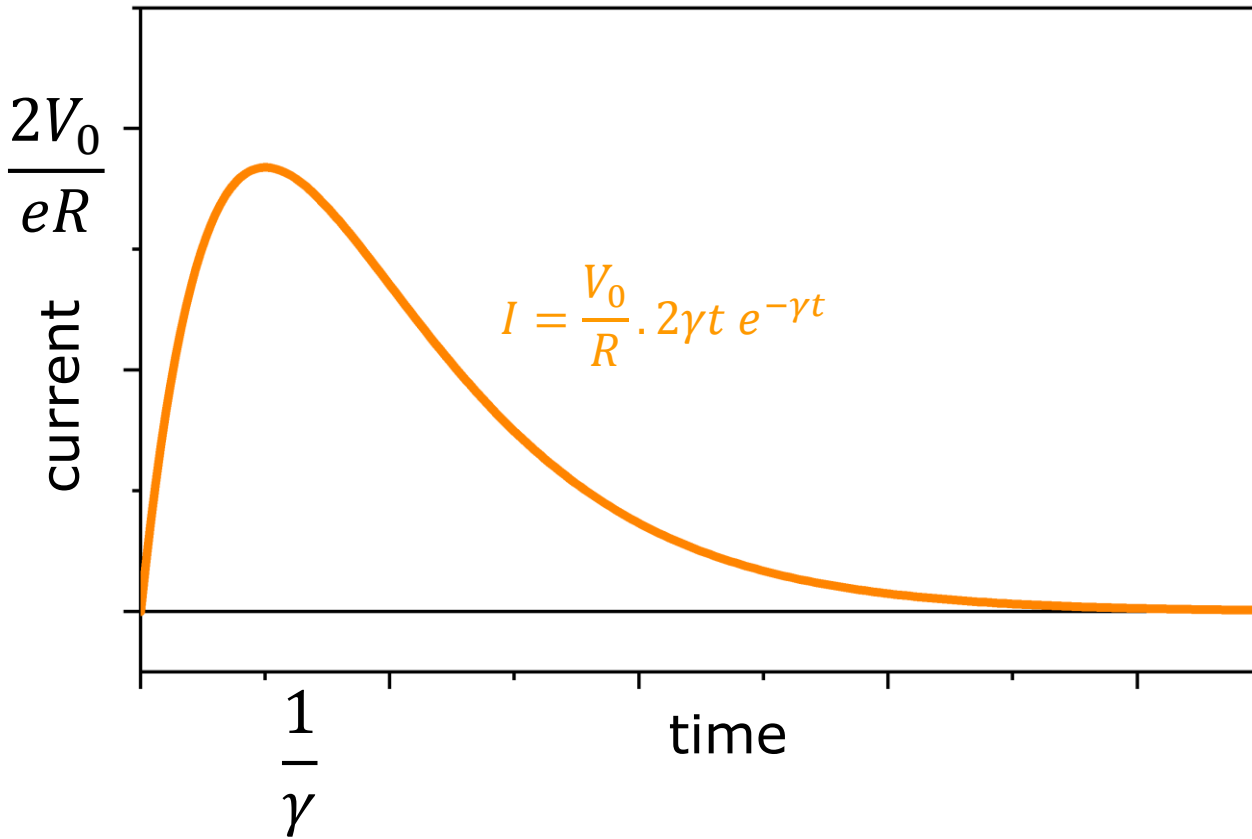

$$\lambda_1 = \lambda_2 = -\gamma$$

Under-damped ($\gamma < \omega_0$)

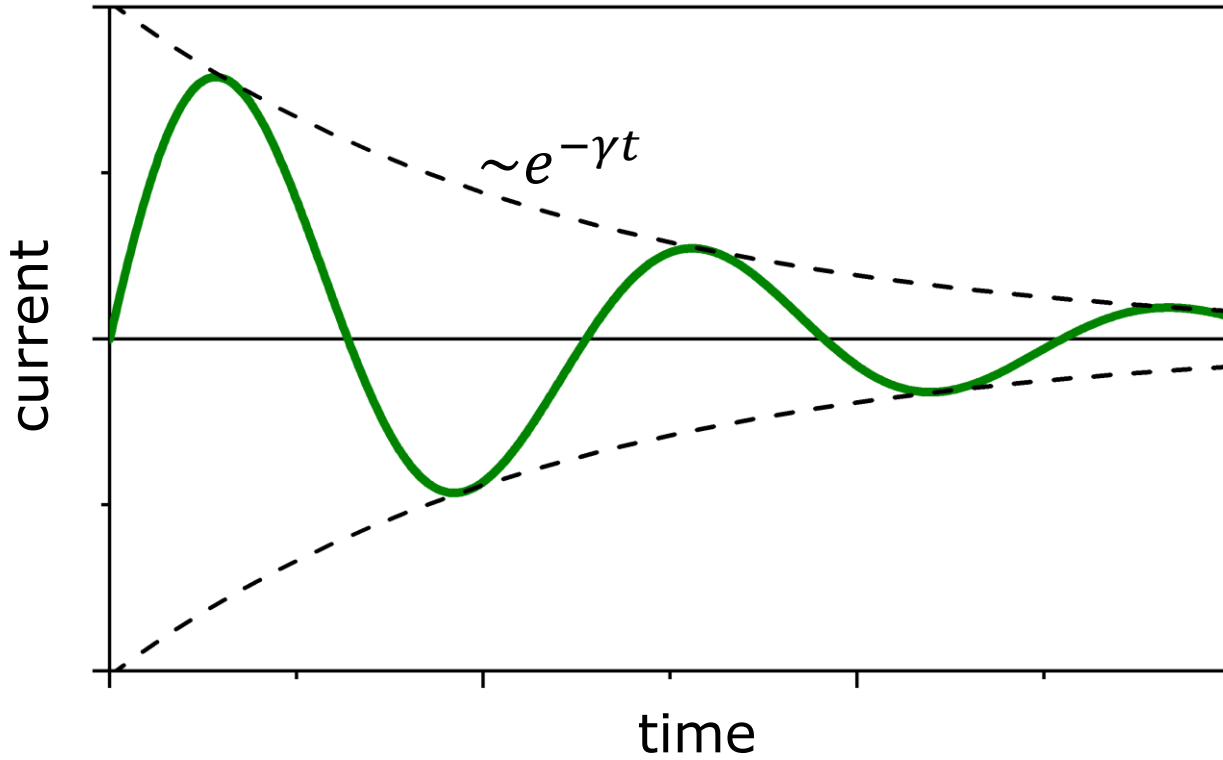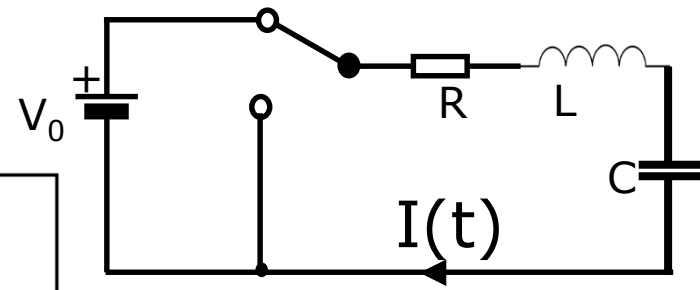

$$\lambda_{1,2} = -\gamma \pm i\sqrt{\omega_0^2 - \gamma^2}$$


$$I = \frac{V_0}{R} \frac{2}{\sqrt{\omega_0^2/\gamma^2 - 1}} e^{-\gamma t} \sin\left(\sqrt{\omega_0^2 - \gamma^2} t\right)$$

Close to ω_0 but not exactly

$$I = V_0 \sqrt{\frac{C}{L}} \frac{1}{\sqrt{1 - \gamma^2/\omega_0^2}} e^{-\gamma t} \sin\left(\sqrt{\omega_0^2 - \gamma^2} t\right)$$

Exam problem

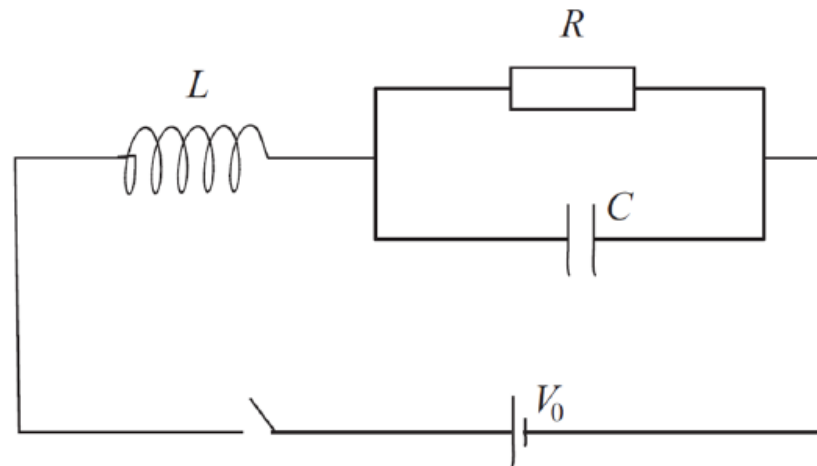b) The same network is connected to a battery, voltage V_0 , as shown below. At time $t = 0$ the capacitor is uncharged and the switch is closed. By solving an appropriate differential equation, show that the current through the resistor is oscillatory provided $L < 4CR^2$. By considering the boundary conditions at $t = 0$ and as $t \rightarrow \infty$, sketch the form of this current as a function of time.



R, L, C circuits

- What if we have more than just one of each?
- What if we don't have switches but have some other input instead?
 - Power from the wall socket comes as a sinusoid, wouldn't it be good to solve such problems?
- **Yes! There is a much better way!**
 - **Stay Tuned for the Unexpected!**