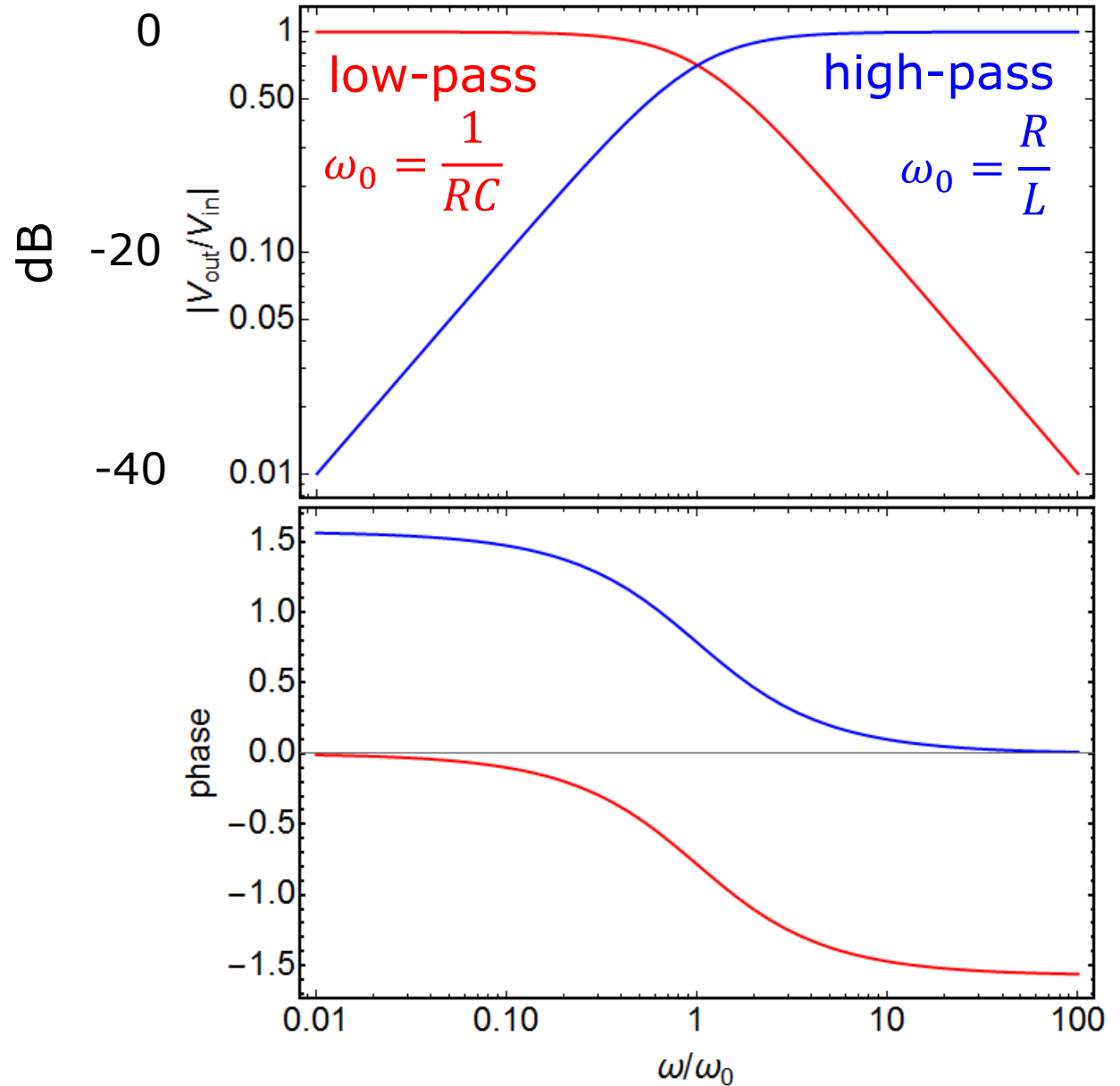


# Recap


$$\text{dB} = 20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$$



# Today: AC circuit analysis

- Band pass filter
- Bridge circuits
- Power dissipation in AC circuits

# Bandpass filter

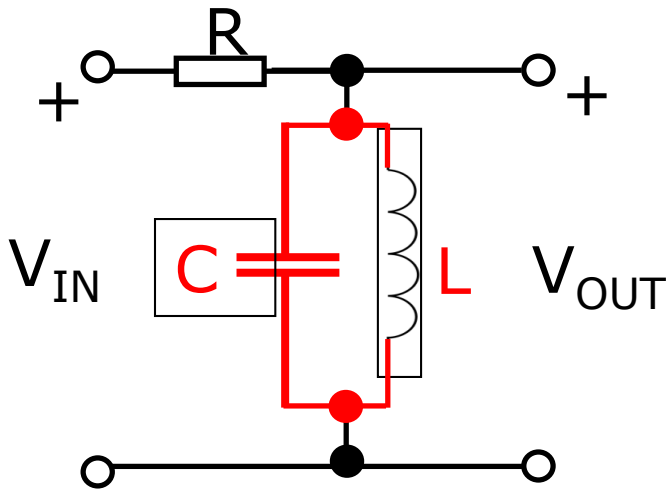

$$\frac{V_{out}}{V_{in}} = \frac{Z_{LC}}{Z_{LC} + R} = \frac{1}{1 + \frac{R}{Z_{LC}}}$$

And we have  $\frac{1}{Z_{LC}} = i\omega C + \frac{1}{i\omega L}$

(Note that at  $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$  we have  $Z_{LC} \rightarrow \infty$ )

So 
$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + iR\left(\omega C - \frac{1}{\omega L}\right)}$$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 1 \text{ for } \omega = \omega_0$$


$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0 \text{ for } \omega \rightarrow 0$$

$$\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0 \text{ for } \omega \rightarrow \infty$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{iR}{L\omega_0} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$
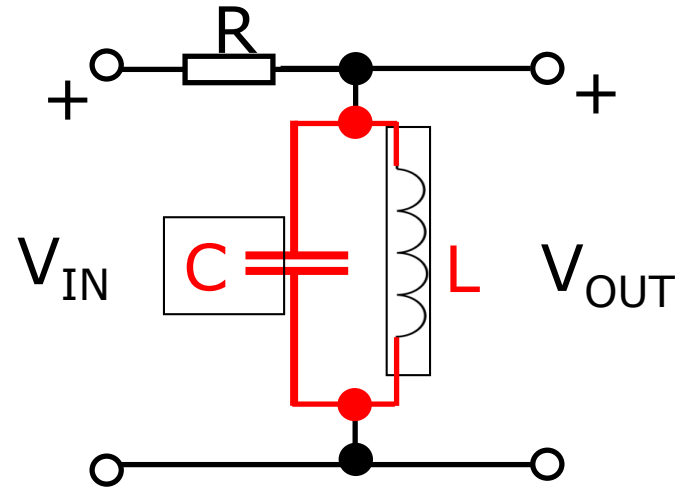
# Bandpass filter


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{iR}{L\omega_0} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$



$Z_{LC} \rightarrow 0$

$Z_{LC} \rightarrow \infty$

$Z_{LC} \rightarrow 0$

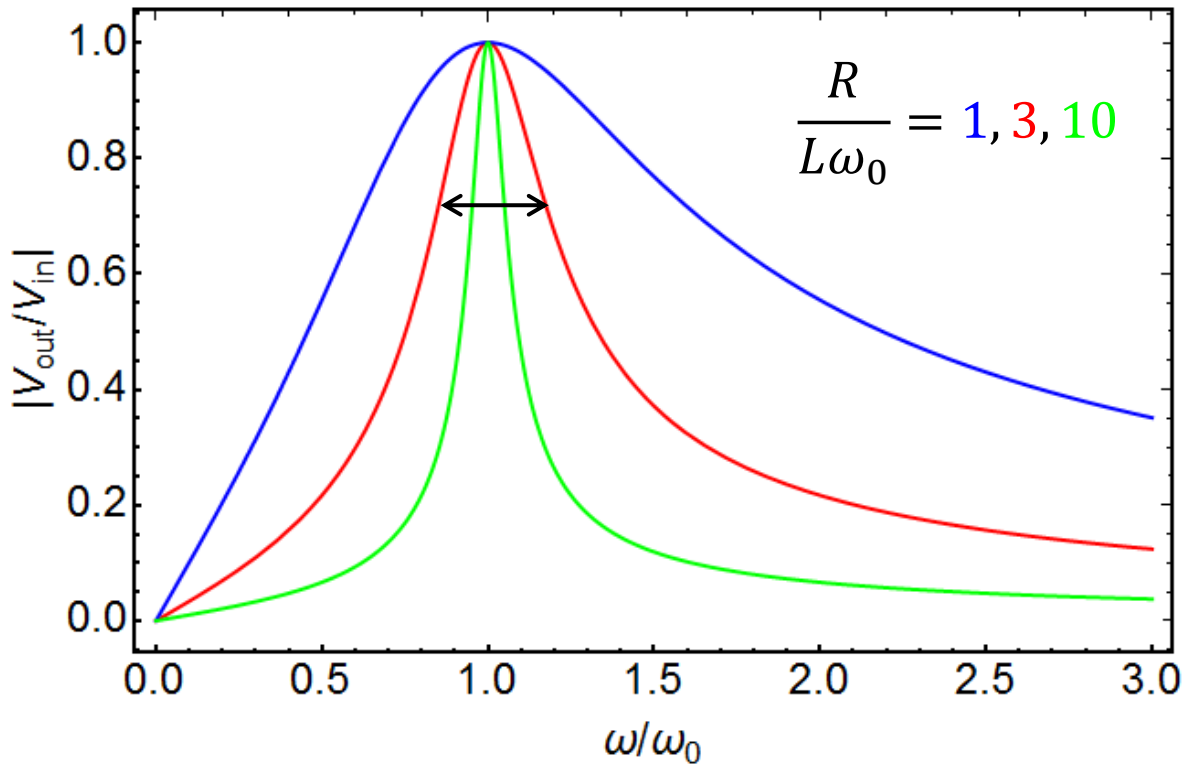

Here larger  $R$  gives sharper feature!!

$$\Delta\omega_{FWHM} = \frac{L\omega_0^2}{R}$$


Quality factor

$$Q = \frac{\omega_0}{\Delta\omega_{FWHM}} = \frac{R}{L\omega_0} = R \sqrt{\frac{C}{L}}$$


# Bandpass filter – Bode plots

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \left( \frac{R}{L\omega_0} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right)^2}}$$
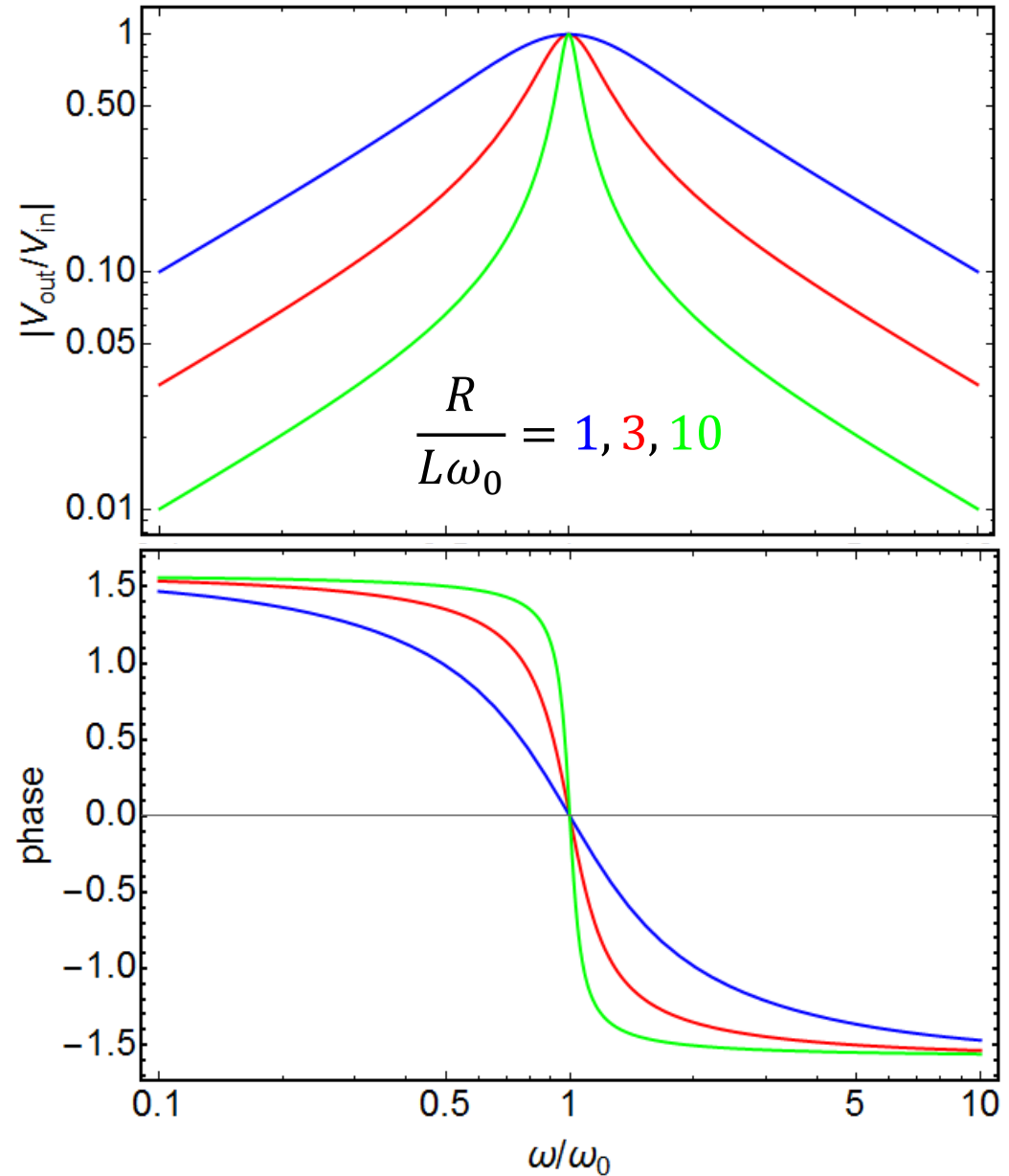
$$\phi = -\arctan \left( \frac{R}{L\omega_0} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right)$$



# Bridge circuits

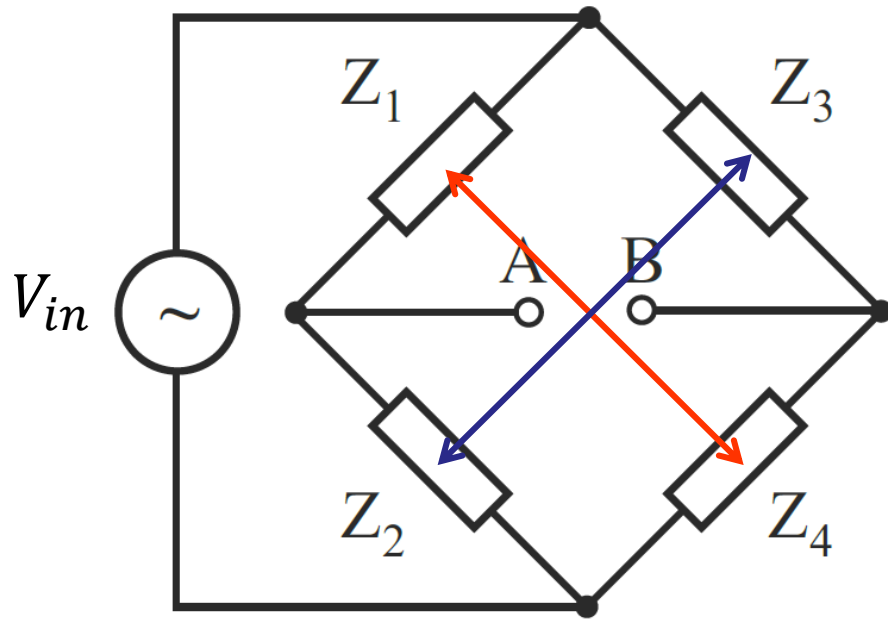

Used to determine an unknown impedance

$$V_A = \frac{Z_2}{Z_1 + Z_2} V_{in}$$

$$V_B = \frac{Z_4}{Z_3 + Z_4} V_{in}$$


Bridge balanced when  $V_{AB} = 0 \rightarrow \frac{Z_2}{Z_1 + Z_2} = \frac{Z_4}{Z_3 + Z_4}$

$$\rightarrow Z_1 Z_4 = Z_2 Z_3$$

(gives 2 equations – real and imaginary parts)

# CP2 September 2003

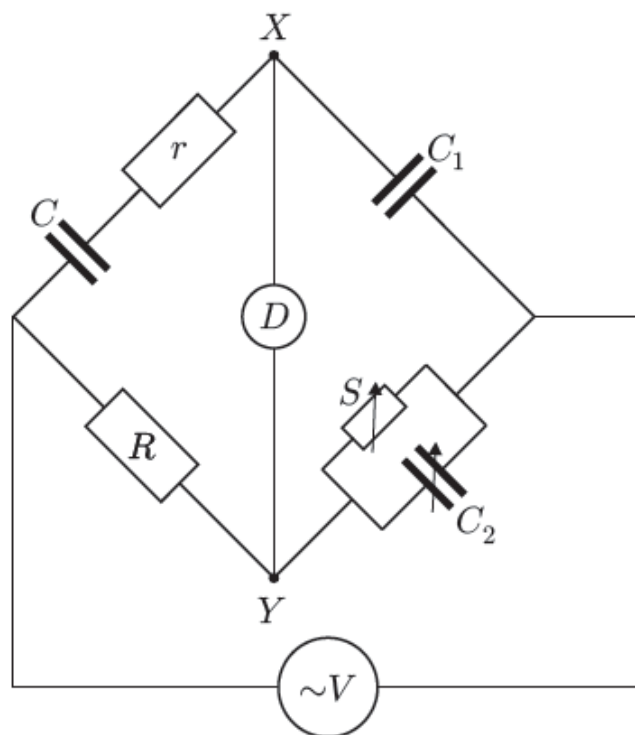9. (i) A Schering bridge is used to determine the capacitance  $C$  and resistance  $r$  of a lossy capacitor. In the diagram below the instrument  $D$  detects when  $X$  and  $Y$  are at the same potential, i.e. the bridge is balanced.



Show that the conditions for balancing the bridge are

$$C = C_1 S / R \quad \text{and} \quad r = C_2 R / C_1 .$$

[10]

# Power in AC circuits

Power into component:  $P = VI$  (real values)

So remember  $P = \text{Re}(\tilde{I}) \times \text{Re}(\tilde{V})$

$$P = I_0 \cos(\omega t) \times I_0 |Z| \cos(\omega t + \phi)$$

Time average  $\rightarrow \langle P \rangle = \frac{1}{2} I_0^2 |Z| \cos(\phi) = \frac{1}{2} I_0^2 \text{Re}(Z)$

Power factor

Or  $\rightarrow \langle P \rangle = \frac{1}{2} V_0 I_0 \cos(\phi) = V_{\text{rms}} I_{\text{rms}} \cos(\phi)$

Resistive load  $Z = R, \cos(\phi) = 1$


Reactive load  $Z = iX, \cos(\phi) = 0$


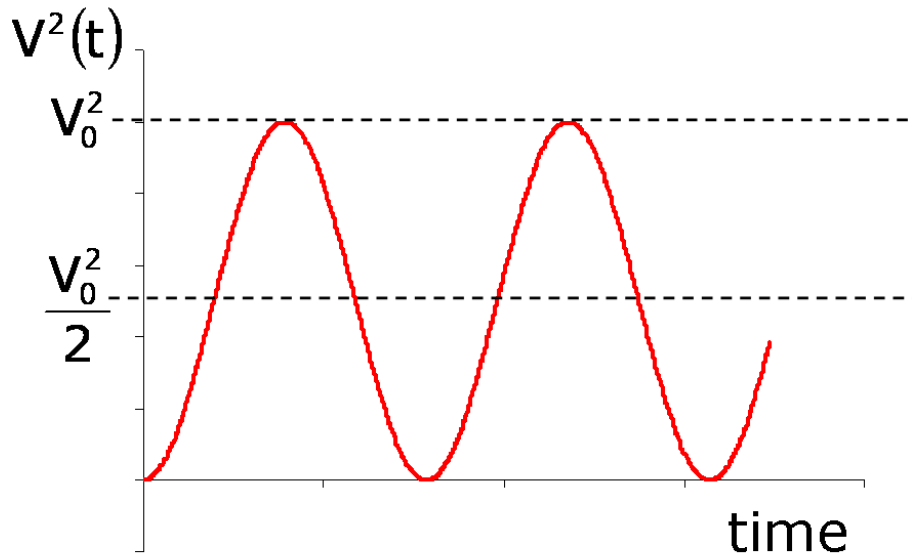
# RMS values

For resistive load  $\langle P \rangle = \langle IV \rangle = \left\langle \frac{V^2}{R} \right\rangle = \frac{V_{\text{rms}}^2}{R}$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$



For sinusoid  $V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$

## CP2 September 2003

(ii) A source of alternating voltage  $V_0 \exp(j\omega t)$  with internal complex impedance  $Z_1 = R_1 + jX_1$  is connected to a load of complex impedance  $Z_2 = R_2 + jX_2$ .

Show that the current through the load is given by

$$I = I_0 \exp[j(\omega t - \phi)],$$

where

$$I_0 = V_0 \left[ (R_1 + R_2)^2 + (X_1 + X_2)^2 \right]^{-1/2},$$

and find an expression for  $\phi$ .

[4]

Hence show that the mean power  $\langle P \rangle$  consumed by the load over one cycle is

$$\langle P \rangle = \frac{1}{2} I_0^2 R_2.$$

[6]