

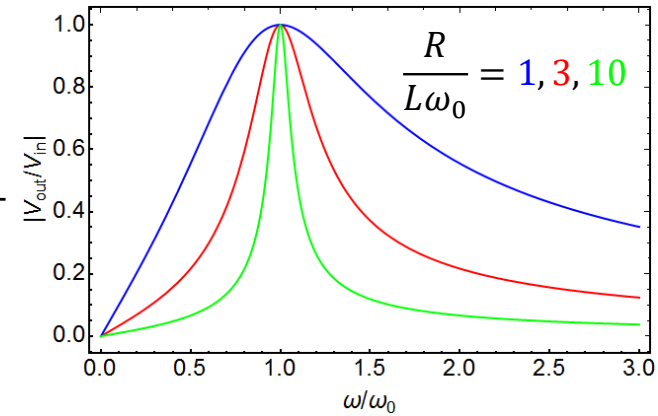


Recap

- Band pass filter

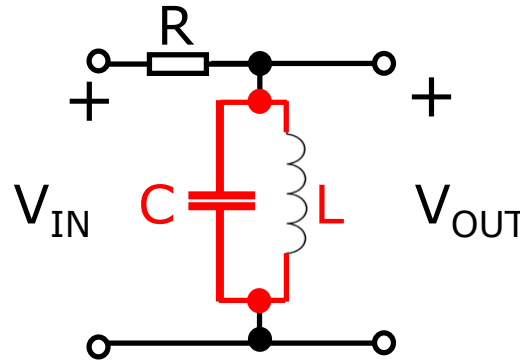

- Bridge circuits

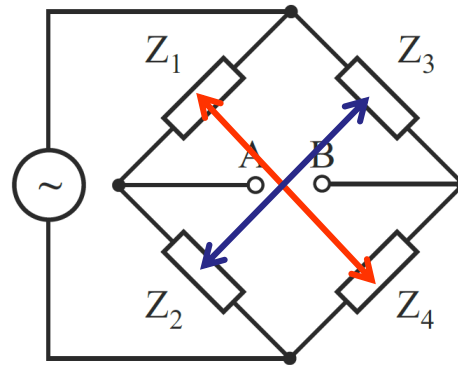

Balanced when

$$Z_1 Z_4 = Z_2 Z_3$$

- Power dissipation in AC circuits





$$\langle P \rangle = \frac{1}{2} I_0^2 \operatorname{Re}(Z) = \frac{1}{2} V_0 I_0 \cos(\phi) = V_{\text{rms}} I_{\text{rms}} \cos(\phi)$$

$$Z = |Z| e^{i\phi}$$


Today

- Op-amps

Operational amplifiers (op-amps)

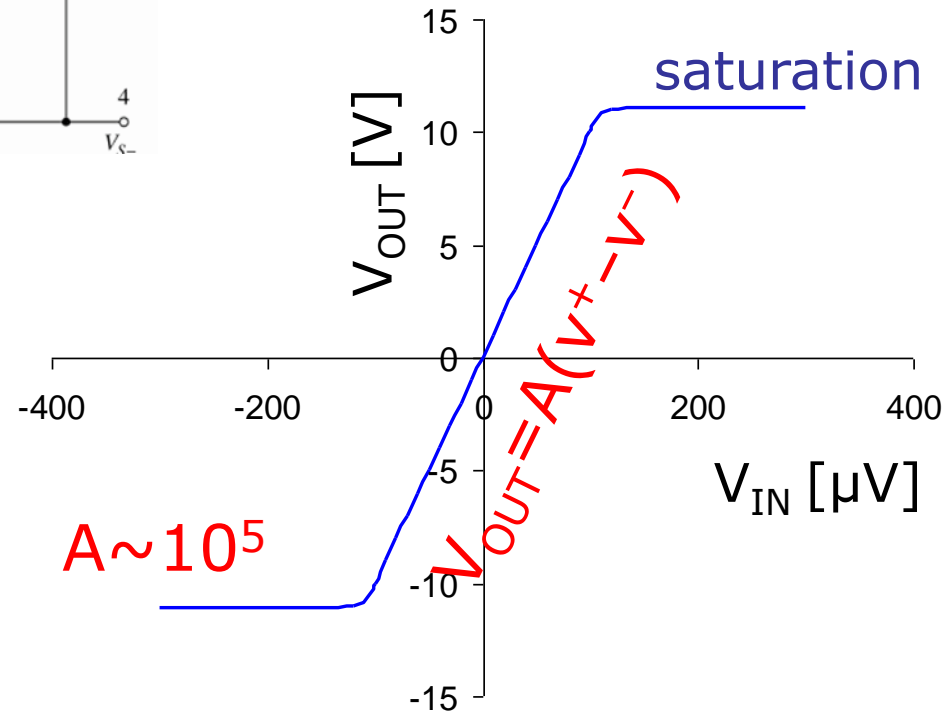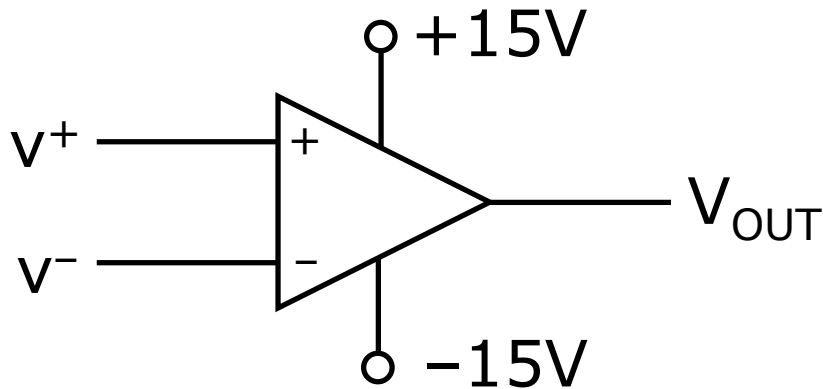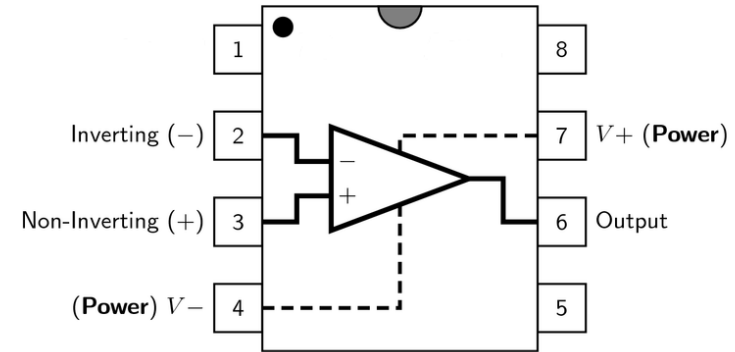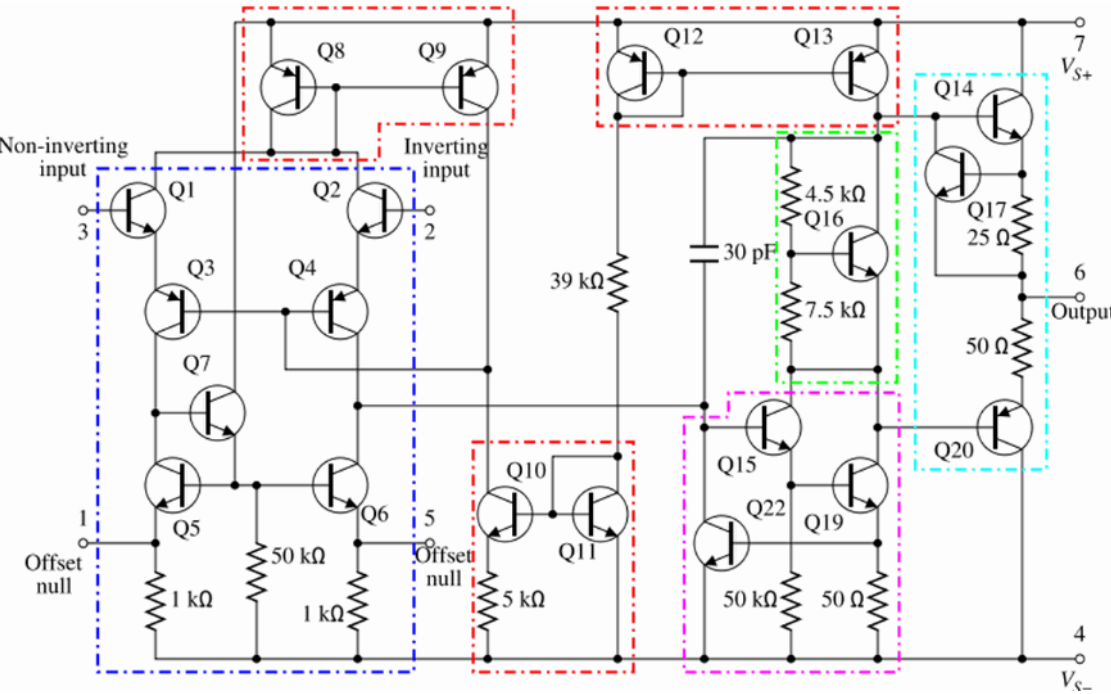

The ideal op-amp

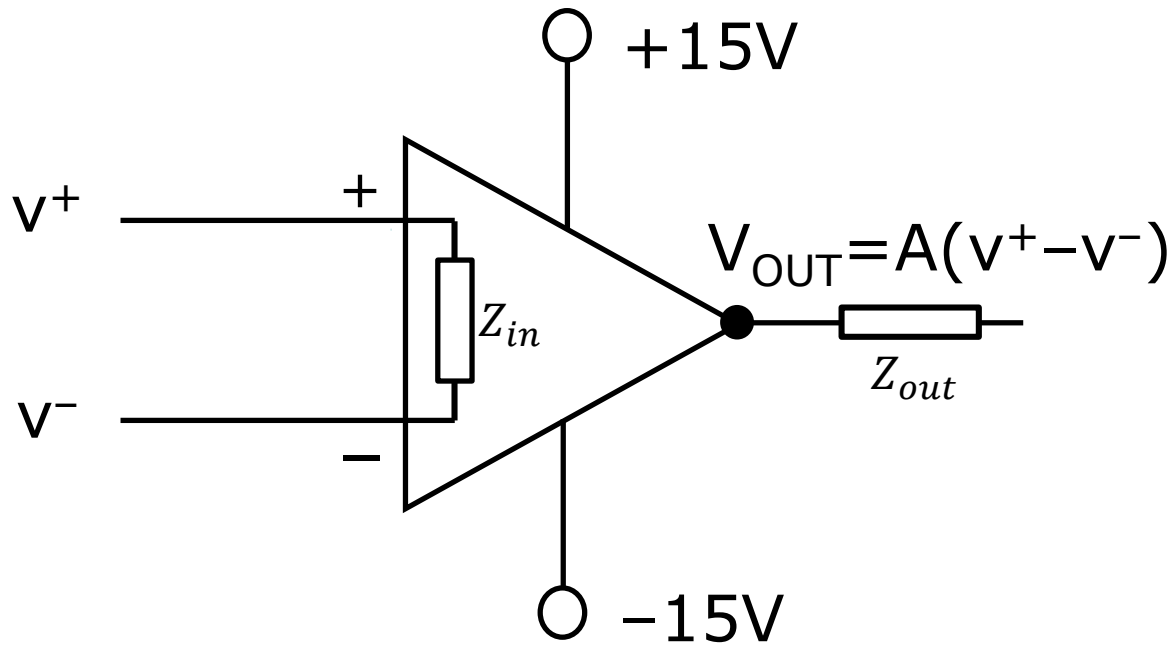

Real

$$Z_{in} \sim 10^8 \Omega$$

$$Z_{out} \sim 100 \Omega$$

$$A \sim 10^5$$

Ideal


$$Z_{in} = \infty \text{ (draws no current)}$$

$$Z_{out} = 0 \text{ (supplies unlimited current)}$$

$$A = \infty \text{ (} v_+ = v_- \text{)}$$

Need feedback

Op-amp Feedback

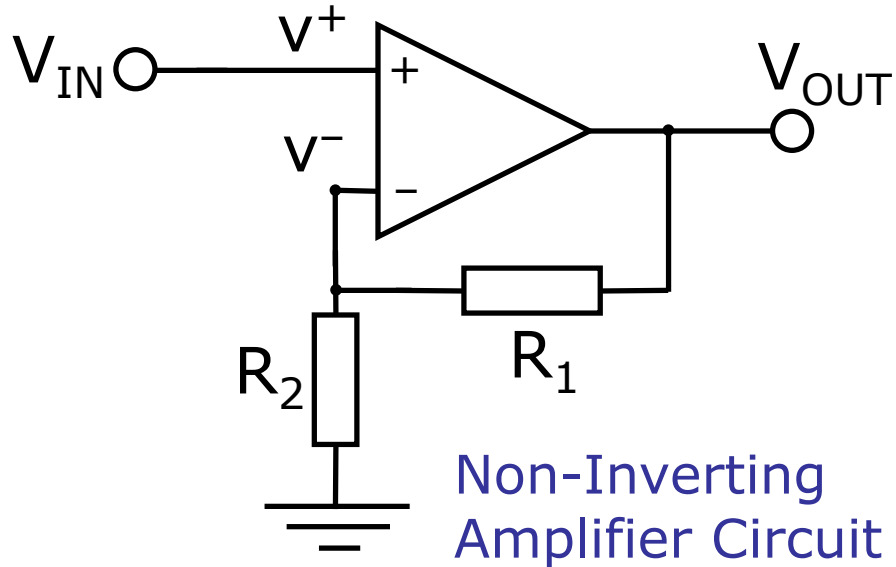

$$V_{OUT} = A(v^+ - v^-)$$

$$V_{OUT} = A \left(V_{IN} - V_{OUT} \frac{R_2}{R_1 + R_2} \right)$$

$$V_{OUT} \left(1 + A \frac{R_2}{R_1 + R_2} \right) = AV_{IN}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + \frac{AR_2}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_2}$$


But feedback must be negative

Op-amp golden rules

- **Golden Rule #1: the inputs draw no current**
Because $Z_{in} = \infty$
- **Golden Rule #2: $V_+ = V_-$**
Because $A = \infty$
This requires negative feedback


Applying these means you can analyse a circuit containing an op-amp without knowing anything about the details of the op-amp

Non-Inverting Amplifier

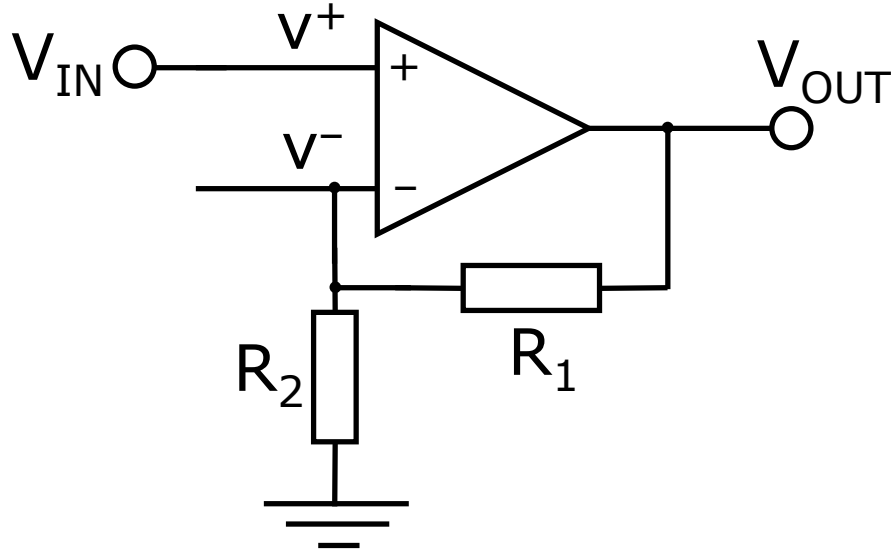


$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_2}$$

Inverting Amplifier

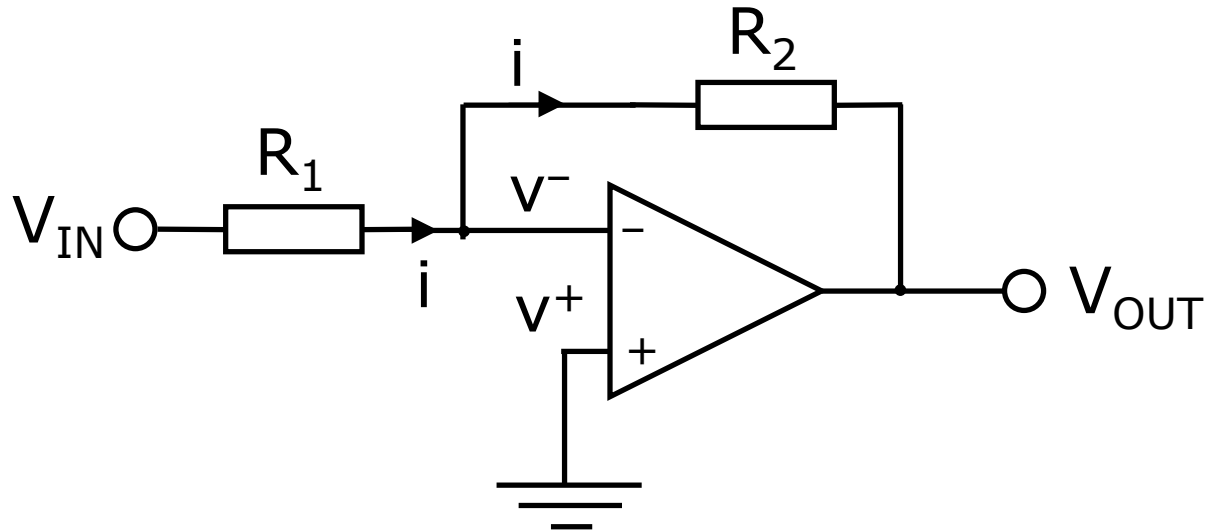


$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

Summing Amplifier

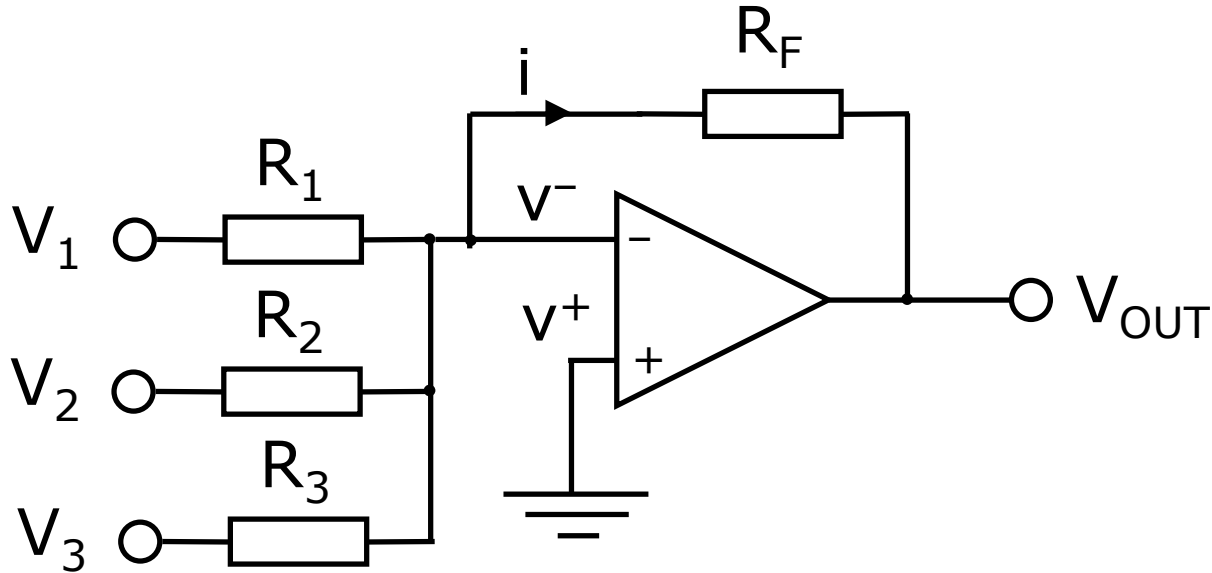

$$V_{out} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

Difference amplifier

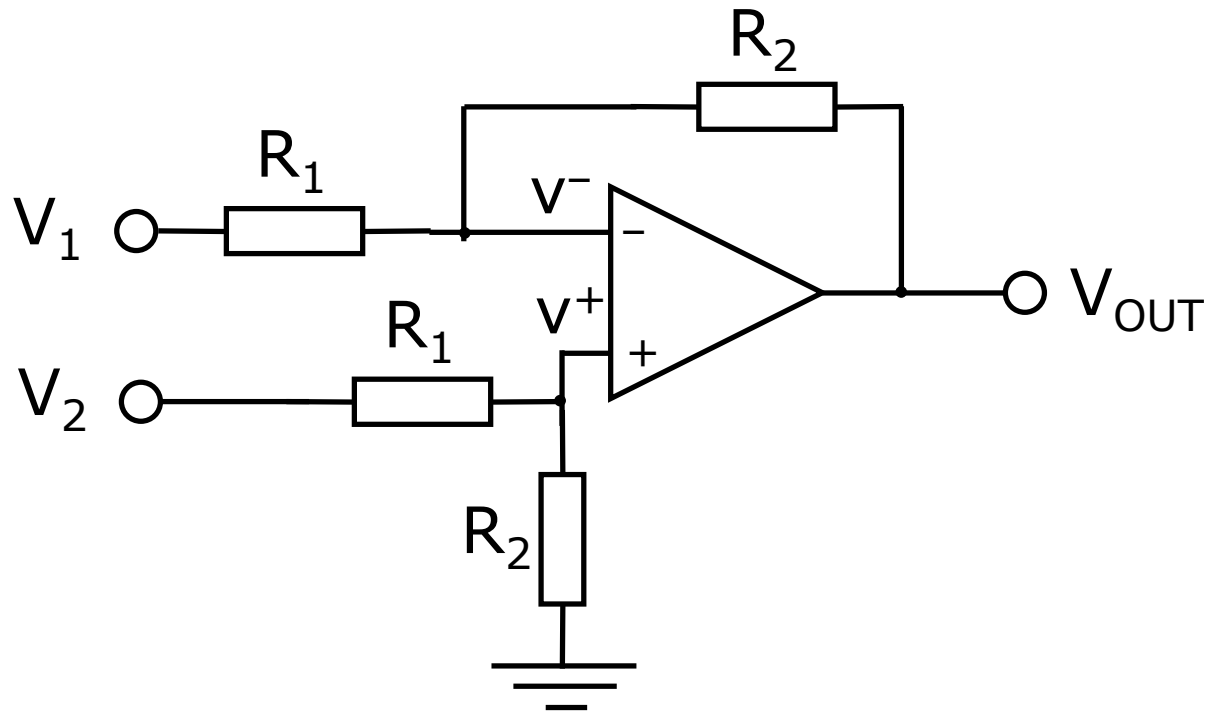

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

