

Recap: Op-amp golden rules

- **Golden Rule #1: the inputs draw no current**
Because $Z_{in} = \infty$
- **Golden Rule #2: $V_+ = V_-$**
Because $A = \infty$
This requires negative feedback


Applying these means you can analyse a circuit containing an op-amp without knowing anything about the details of the op-amp

Today

More examples


- Difference amplifier
- Integrator
- Differentiator
- AC analysis
- Using saturation

Difference amplifier

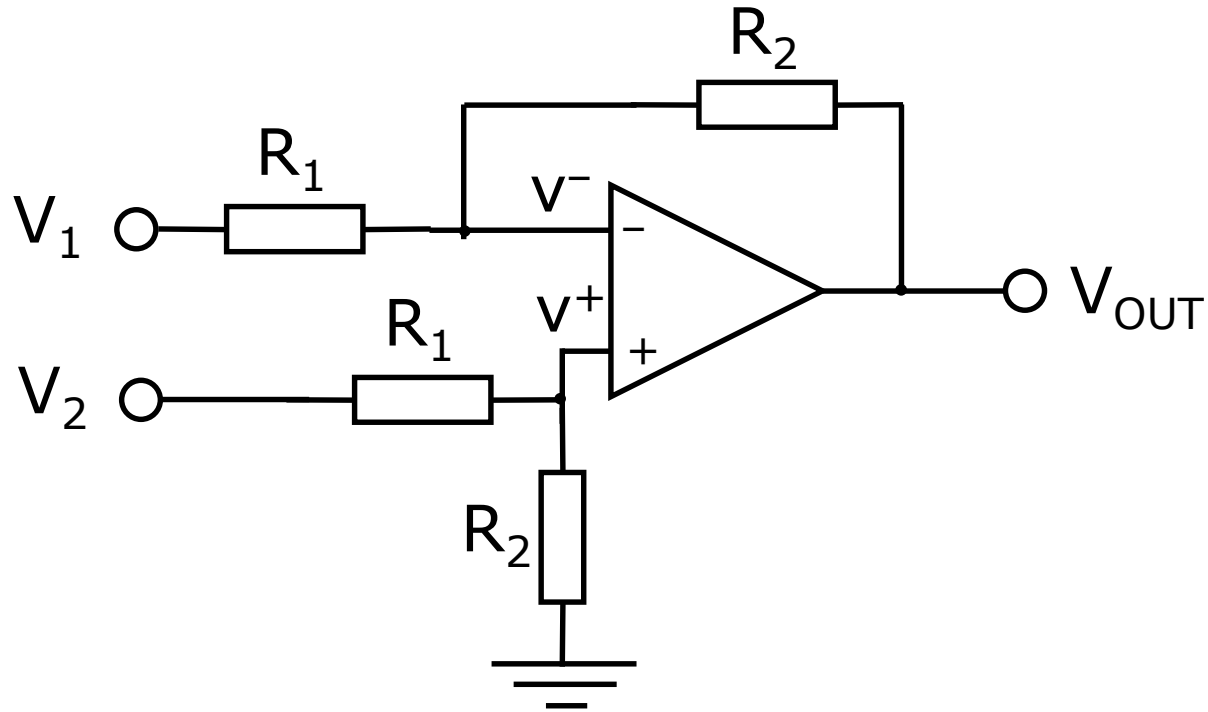


$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$

Op-amp Integrator

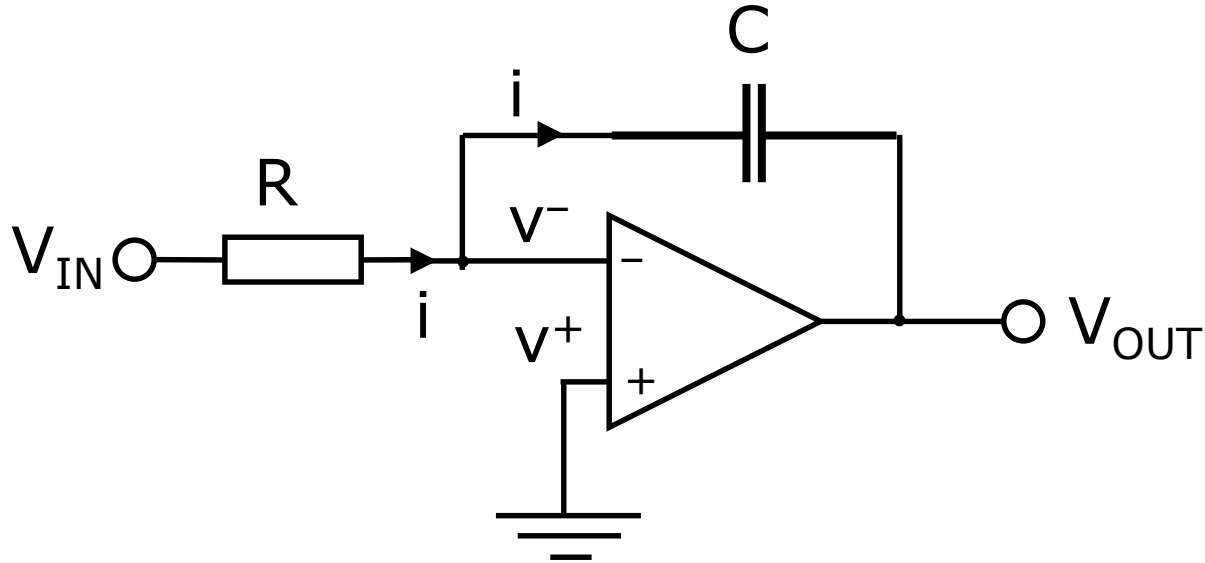


$$V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt$$


Op-amp Differentiator

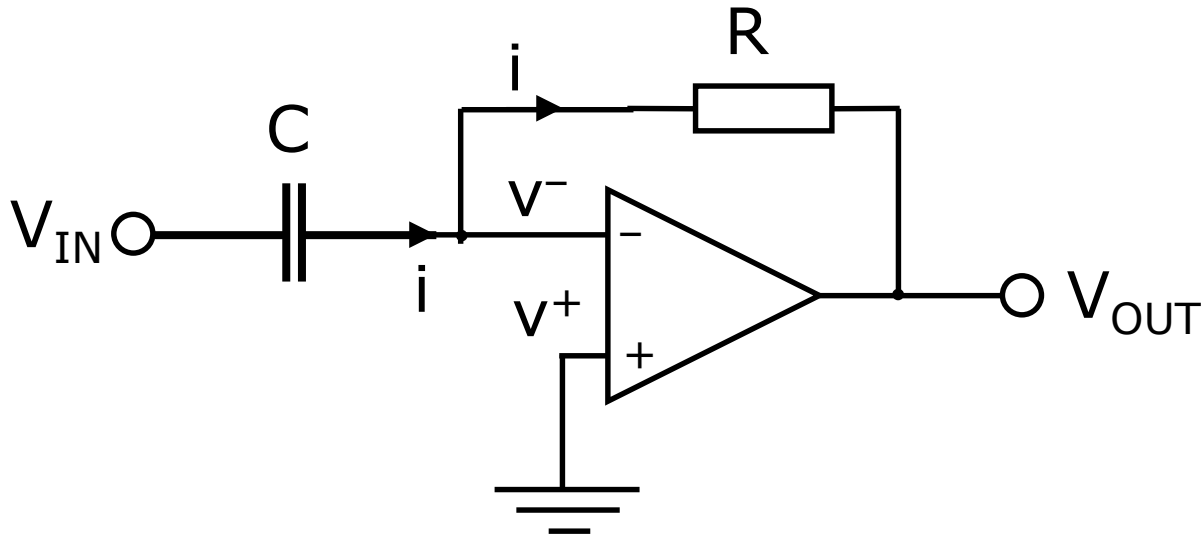

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

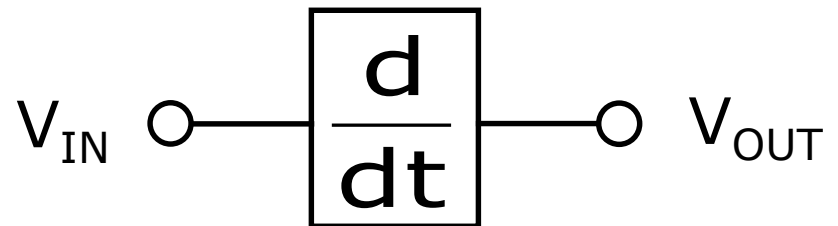

Complex analysis

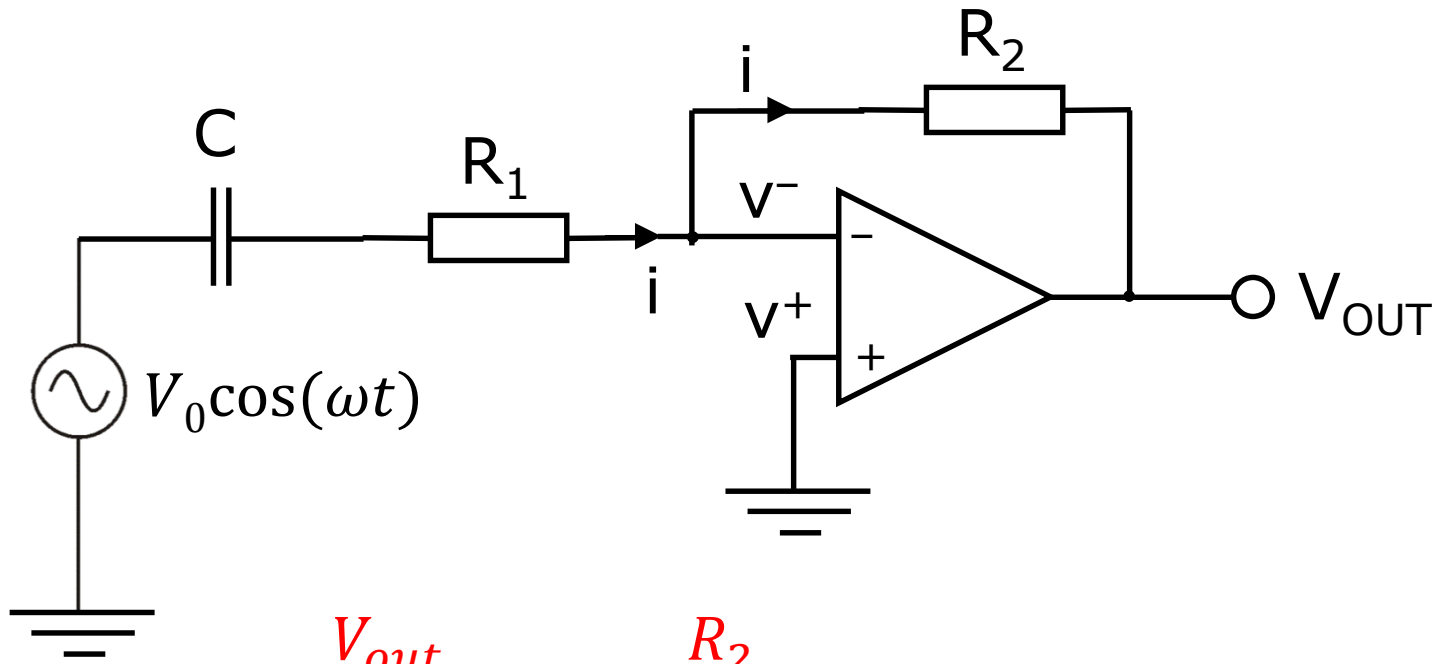


$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1 + \frac{1}{i \omega C}}$$

High pass filter

$$\omega \rightarrow 0 \quad \left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0$$

$$\omega \rightarrow \infty \quad \left| \frac{V_{out}}{V_{in}} \right| \rightarrow \frac{R_2}{R_1}$$


Bridge circuits

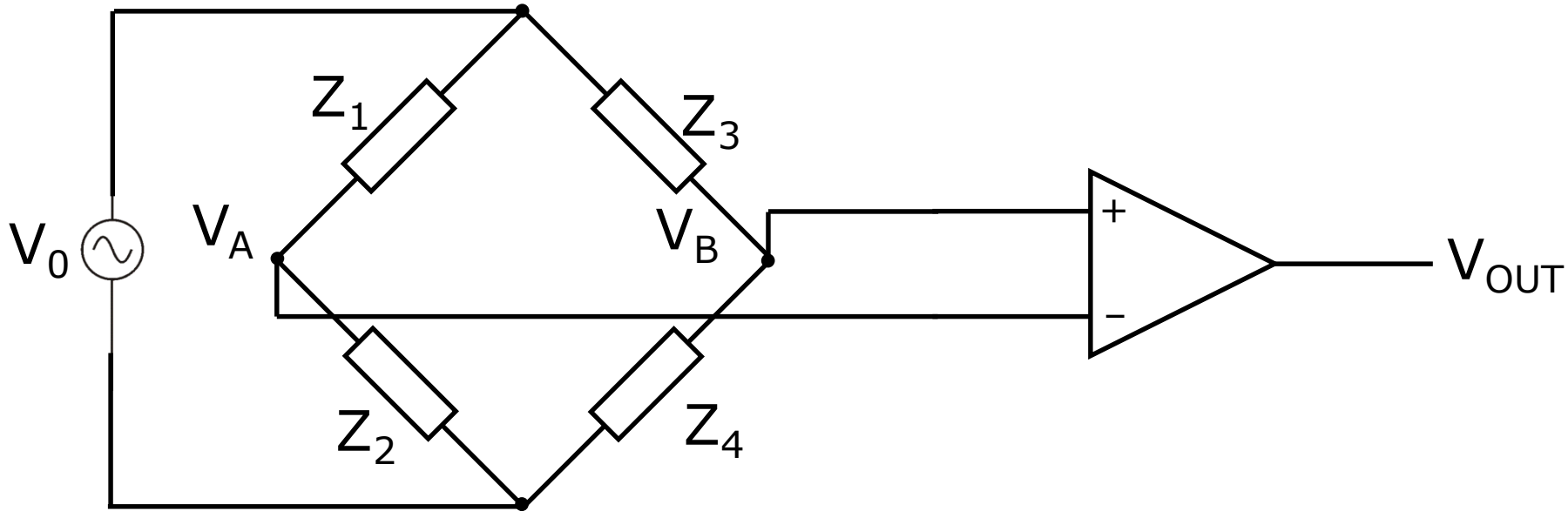

Bridge balanced when $V_A - V_B = 0$

$$Z_2 Z_3 = Z_4 Z_1$$

Exploiting op-amp saturation

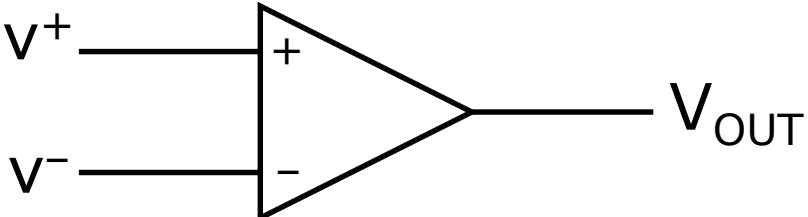


$V_{OUT} = A(v^+ - v^-)$


$A \rightarrow \infty$

Saturation voltage
↓

$V_{OUT} = +V_{Sat}$	$v^+ > v^-$
$V_{OUT} = -V_{Sat}$	$v^+ < v^-$

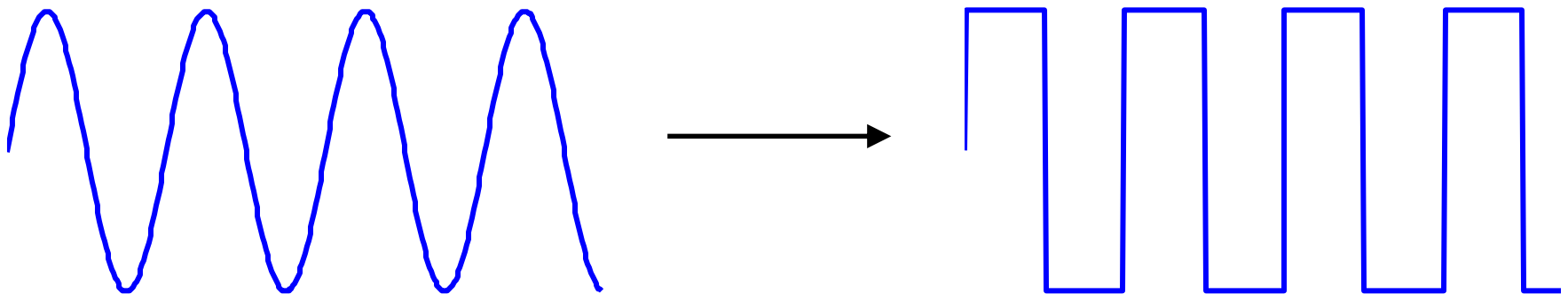

Oscillator (non ideal)

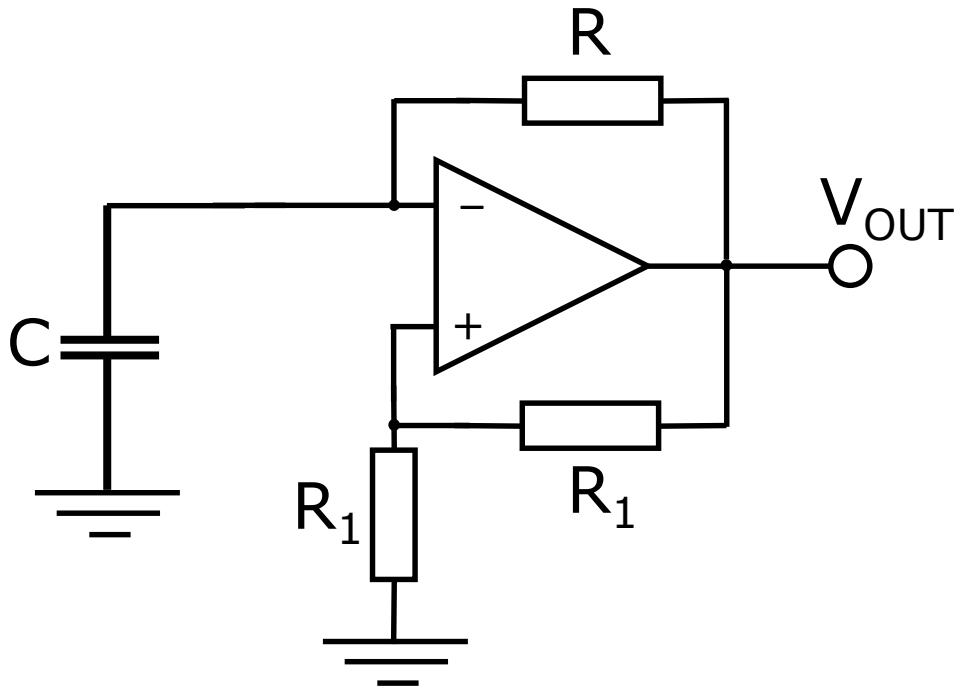

What does this circuit do?

Op-amp applications

Building block of analogue electronics

Signal amplifiers

Audio amplifiers

Integrators / differentiators

Voltage / current sources

Active filters

Oscillators

Digital-analogue and analogue-digital convertors