

Recap

- Capacitors store charge; they resist a change of voltage

$$V = \frac{Q}{C} \quad W = \frac{1}{2} CV^2$$

- Inductors oppose a change in current

$$V = L \frac{dI}{dt} \quad W = \frac{1}{2} LI^2$$

- Transient circuits

RC in series – decays to long-time values with $\tau = RC$


RL in series – decays to long-time values with $\tau = \frac{L}{R}$

LCR series – damped s.h.m. with $\omega_0 = \frac{1}{\sqrt{LC}}$ and $\gamma = \frac{R}{2L}$


Over ($\gamma > \omega_0$), critical ($\gamma = \omega_0$) and under ($\gamma < \omega_0$) damped

Today: AC circuit analysis

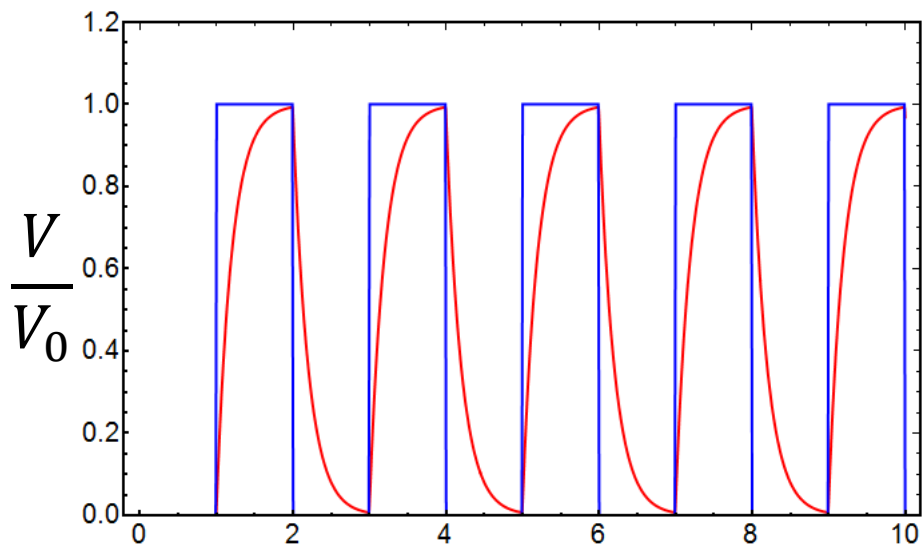
- LCR circuits - what if we don't have switches but have some other input instead?
 - E.g. sinusoidal input voltages (like the power from the wall)
- Response of resistors, capacitors and inductors to AC sources
- Complex impedance



$T \approx \tau_c$

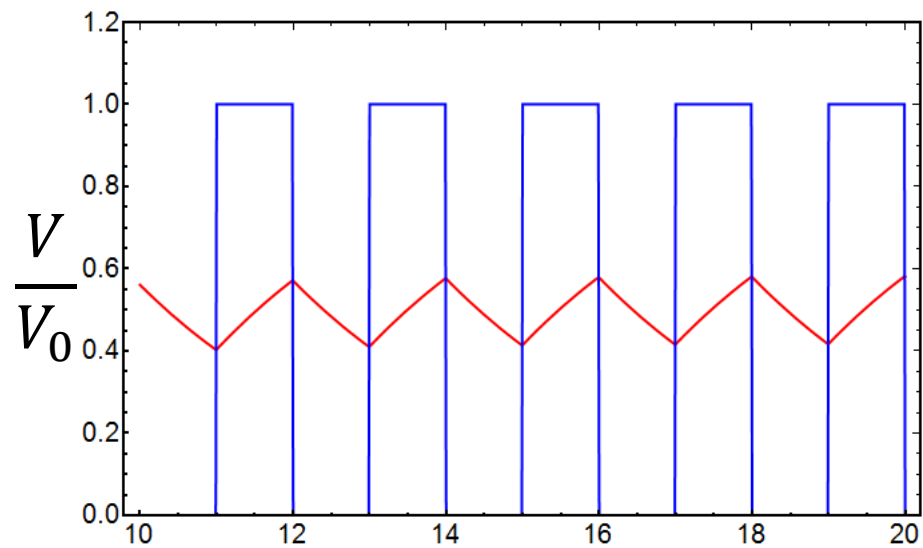


$T \gg \tau_c$

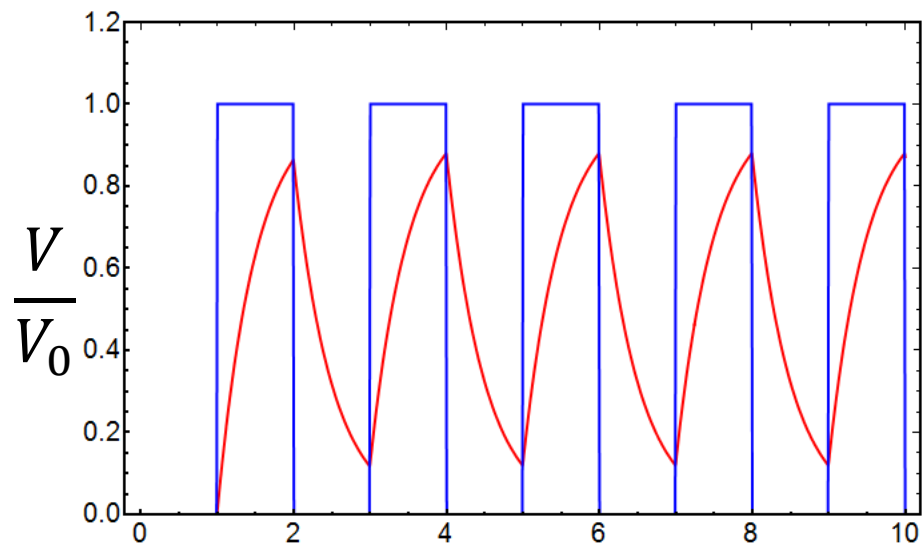

$T \ll \tau_c$

Sinusoidal voltages / currents

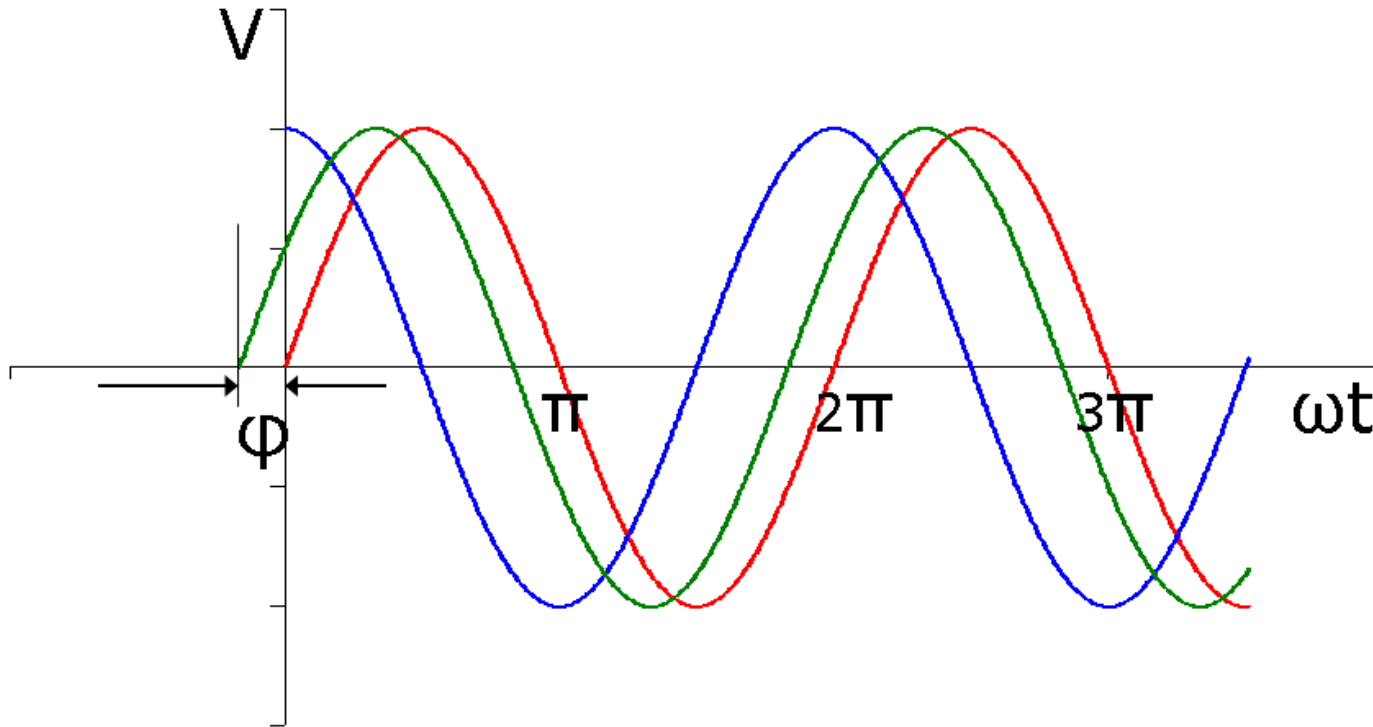

Amplitude

$$V = V_0 \sin(\omega t)$$


Phase

$$V = V_0 \cos(\omega t)$$

$$V = V_0 \sin(\omega t + \varphi)$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$


Apply AC current to a resistor...

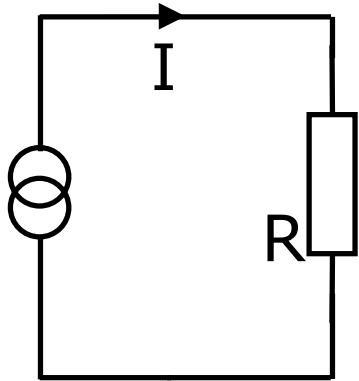

$$I = I_0 \cos(\omega t)$$

$$V_R = RI = RI_0 \cos(\omega t)$$

...capacitor...

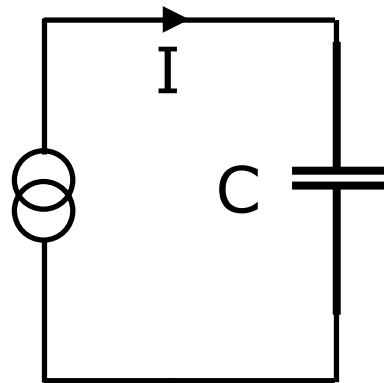


$$V_C = \frac{Q}{C} = \frac{1}{C} \int I_0 \cos(\omega t) dt$$

$$= \frac{1}{\omega C} I_0 \sin(\omega t)$$

$$= \frac{1}{\omega C} I_0 \cos\left(\omega t - \frac{\pi}{2}\right)$$

...and inductor

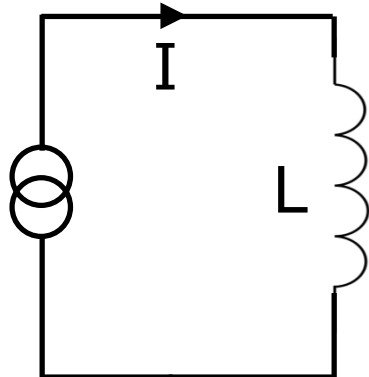


$$V_L = L \frac{dI}{dt} = -\omega L I_0 \sin(\omega t) = \omega L I_0 \cos\left(\omega t + \frac{\pi}{2}\right)$$

Voltage lags current by $\pi/2$

Voltage leads current by $\pi/2$

Adding voltages

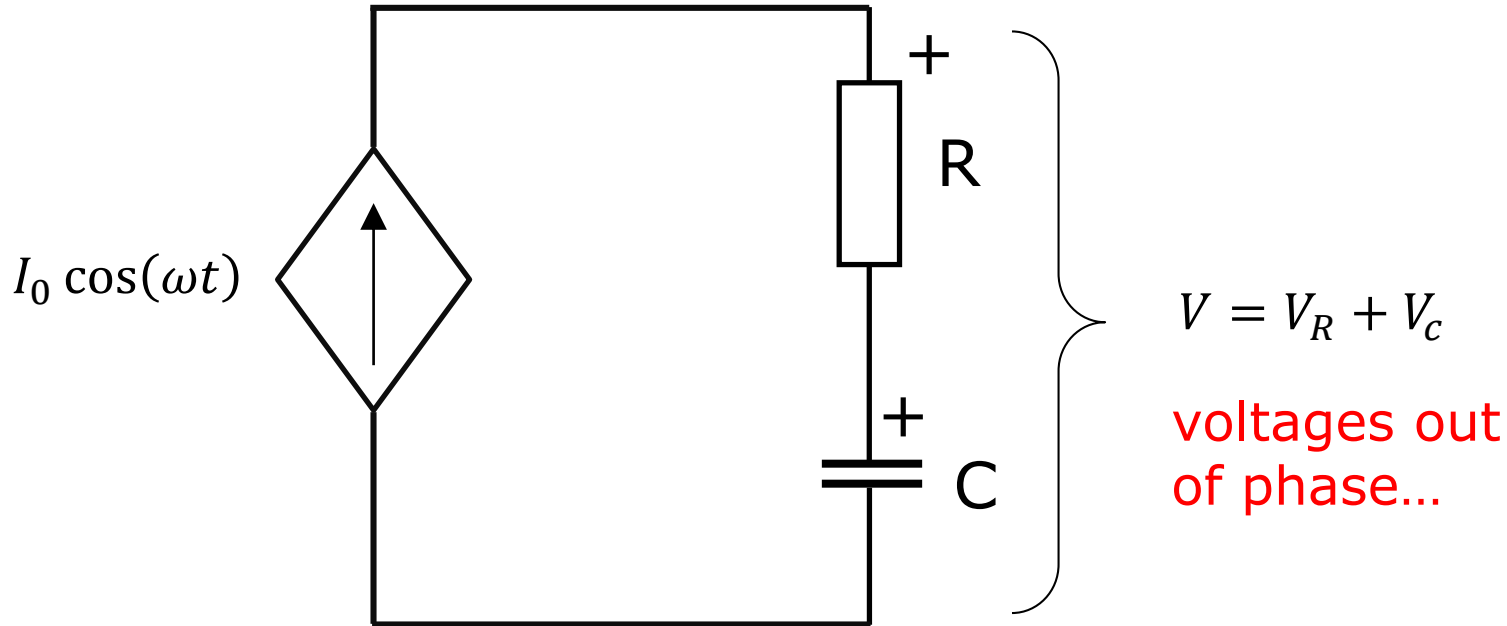

$$V = I_0 \left(R \cos(\omega t) + \frac{1}{\omega C} \sin(\omega t) \right)$$

$$V = I_0 A \cos(\omega t + \phi)$$

$$A = \sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}$$

$$\phi = -\arctan \left(\frac{1}{\omega R C} \right)$$

Complex Impedance

Tells you both the **amplitude** and **phase** of the voltage response when applying an oscillating current

$$Z = Ae^{i\phi} = |Z|e^{i\phi}$$

Resistor $Z_R = R$

Capacitor $Z_C = \frac{1}{i\omega C}$

Inductor $Z_L = i\omega L$

$$Z = R + iX$$

Resistance Reactance

Generalised Ohm's law

$$I = I_0 \cos(\omega t) = \operatorname{Re}(I_0 e^{i\omega t}) = \operatorname{Re}(\tilde{I})$$

$$V = I_0 |Z| \cos(\omega t + \phi) = \operatorname{Re}(I_0 |Z| e^{i(\omega t + \phi)})$$

$$V_0 \cos(\omega t + \phi) = \operatorname{Re}(I_0 |Z| e^{i\phi} e^{i\omega t})$$

$$\operatorname{Re}(V_0 e^{i(\omega t + \phi)}) = \operatorname{Re}(I_0 Z e^{i\omega t})$$

$$\operatorname{Re}(\tilde{V}) = \operatorname{Re}(\tilde{I} Z)$$

$$\tilde{V} = \tilde{I} Z$$

\tilde{V} and \tilde{I} are **phasors**

Phasors

- Rotate around in complex plane
- Actual voltage is projection onto real axis



$$\tilde{V} = \tilde{I}Z$$

$$\tilde{I} = \frac{\tilde{V}}{Z}$$


$$|\tilde{V}| = |Z||\tilde{I}|$$

$$\text{Arg}(\tilde{V}) = \text{Arg}(Z) + \text{Arg}(\tilde{I})$$

Series impedances

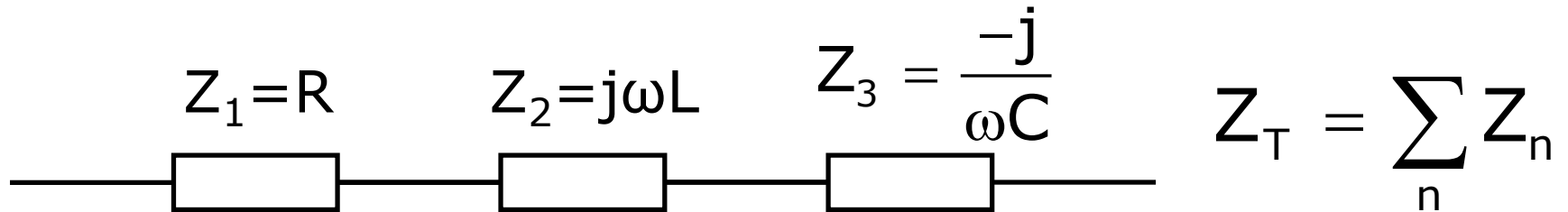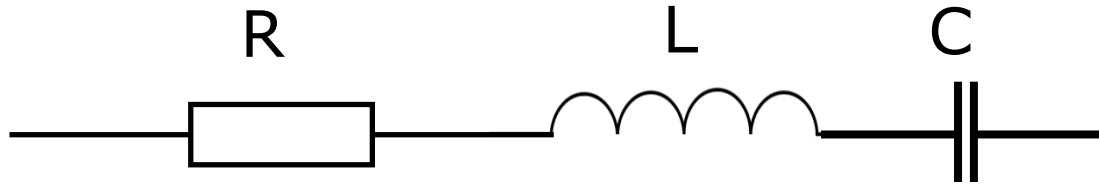


Parallel impedances

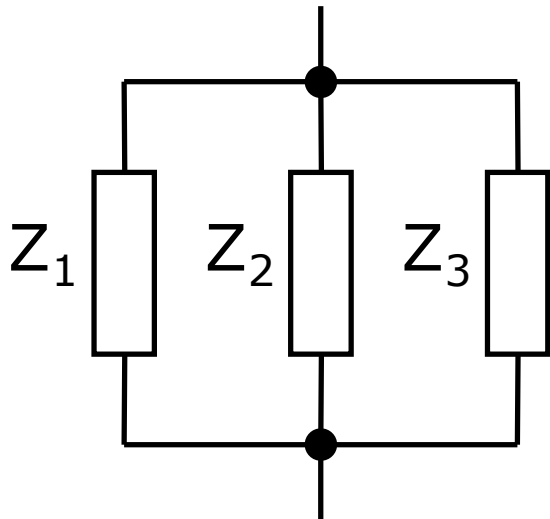

$$\frac{1}{Z_T} = \sum_n \frac{1}{Z_n}$$
$$= \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} \dots$$

Example

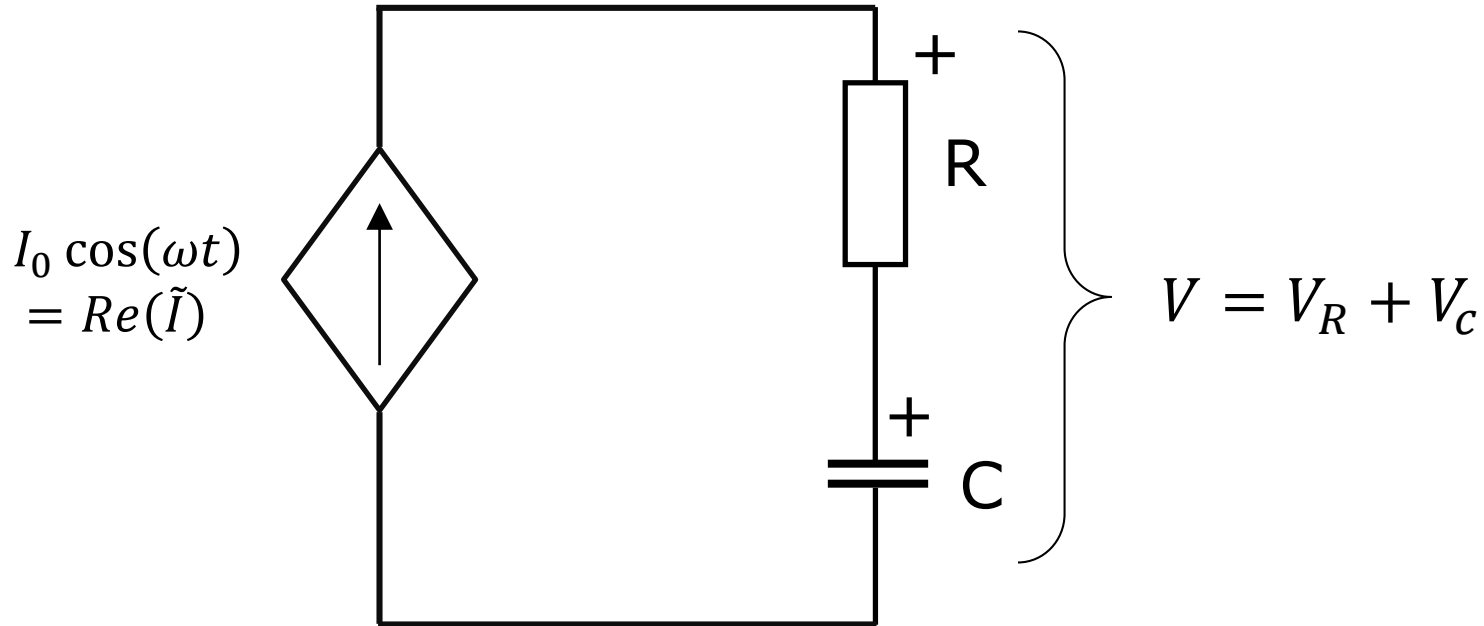

$$\tilde{V} = \tilde{I}Z = \tilde{I} \left(R - \frac{i}{\omega C} \right)$$

$$V = \text{Re}(\tilde{V}) = I_0 |Z| \cos(\omega t + \phi)$$

$$|Z| = \sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}$$

$$\phi = -\arctan \left(\frac{1}{\omega RC} \right)$$